

Assignment - 02

Name : Md. Farhan Ishmam
Std ID : 180041120
Course Name : Digital electronics and Pulse Techniques
Course Number : FEE ~~4383~~ 4483
Submission Date : 28-10-20

10.1.

The given circuit resembles an inverting amplifier of the OP amp. We know, $V_o = -\frac{R_f}{R_1} V_i$ for inverting amplifier.

Here, $R_f = 250 \text{ k}\Omega = 2.5 \times 10^5 \Omega$

$$R_1 = 20 \text{ k}\Omega = 2 \times 10^4 \Omega$$

$$V_i = 1.5 \text{ V}$$

$$\text{So, } V_o = -\frac{R_f}{R_1} \times V_i = \frac{2.5 \times 10^5}{2 \times 10^4} \times 1.5 \text{ V}$$

$$\therefore V_o = -18.75 \text{ V}$$

Ans: -18.75 V

10.2.

The given circuit resembles an inverting amplifier. We know, $V_o = -\frac{R_f}{R_1} V_i$ for inverting amplifier.

Given, $R_f = \cancel{250 \text{ k}\Omega} 200 \text{ k}\Omega = 2 \times 10^5 \Omega$

$$R_1 = 20 \text{ k}\Omega = 2 \times 10^4 \Omega$$

V_i has a range from 0.1 to 0.5 V .

For, $V_i = 0.1 \text{ V}$,

$$V_o = -\frac{R_f}{R_1} V_i = \frac{2 \times 10^5}{2 \times 10^4} \times 0.1 = -1 \text{ V}$$

For, $V_i = 0.5 \text{ V}$,

$$V_o = -\frac{R_f}{R_1} V_i = \frac{2 \times 10^5}{2 \times 10^4} \times 0.5 = -5 \text{ V}$$

Ans: The range of out put voltage is from
-1V to -5V.

10.5.

The circuit in the figure is a non-inverting amplifier.
The output voltage is

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

$$\text{Given, } R_f = 360 \text{ k}\Omega = 3.6 \times 10^5 \Omega$$

$$R_i = 12 \text{ k}\Omega = 1.2 \times 10^4 \Omega$$

$$V_i = -0.3 \text{ V.}$$

$$\begin{aligned} \therefore V_o &= \left(1 + \frac{R_f}{R_i}\right) V_i \\ &= \left(1 + \frac{3.6 \times 10^5}{1.2 \times 10^4}\right) \times (-0.3) \\ &= (1 + 30) \times (-0.3) \\ &= -9.3 \text{ V} \end{aligned}$$

Ans: -9.3 V

10.6.

The given circuit resembles a non-inverting amplifier.
The output formula is $V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$

$$\text{Given, } R_f = 3.6 \times 10^5 \Omega$$

$$R_i = 1.2 \times 10^4 \Omega$$

$$V_o = 2.4 \text{ V}$$

$$\text{Now, } V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

$$\Rightarrow V_i = \frac{V_o}{1 + \frac{R_f}{R_i}}$$

$$= \frac{2.4}{1 + \frac{3.6 \times 10^5}{1.2 \times 10^4}}$$

$$= \frac{2.4}{1 + \frac{3.6 \times 10^5}{1.2 \times 10^4}}$$

$$= \frac{2.4}{31} = 0.07742 \text{ V}$$

$$= 77.42 \text{ mV}$$

Ans: 77.42 mV

10.7.

The network resembles a non-inverting amplifier.
The output voltage is given by

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

Given, $R_f = 2 \times 10^5 \Omega$

$$R_i = 10 \times 10^3 + R_v$$

$$V_i = 0.5 \text{ V}$$

Setting R_v to minimum value or 0Ω ,

$$R_i = 10 \times 10^3 + 0 = 10^4 \Omega$$

$$\therefore V_o = \left(1 + \frac{2 \times 10^5}{10^4}\right) \times 0.5 = 10.5 \text{ V}$$

Setting R_v to maximum value or $10 \text{ k}\Omega$,

$$R_i = 10 \times 10^3 + 10 \times 10^3 = 20 \times 10^3$$

$$\therefore V_o = \left(1 + \frac{2 \times 10^5}{20 \times 10^3}\right) \times 0.5 = 5.5 \text{ V}$$

Ans: The output voltage will be in range
5.5 V to 10.5 V.

10.8.

The given circuit resembles a summing amplifier

The formula for output voltage is

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$

Given, $R_f = 330 \times 10^3 \Omega$

$$R_1 = 33 \times 10^3 \Omega$$

$$R_2 = 22 \times 10^3 \Omega$$

$$R_3 = 12 \times 10^3 \Omega$$

$$V_1 = 0.2 \text{ V}$$

$$V_2 = -0.5 \text{ V}$$

$$V_3 = 0.8 \text{ V}$$

$$V_o = -\left(\frac{330 \times 10^3}{33 \times 10^3} \times 0.2 + \frac{330 \times 10^3}{22 \times 10^3} \times (-0.5) + \frac{330 \times 10^3}{12 \times 10^3} \times 0.8\right)$$

$$= -(2 - 7.5 + 22)$$

$$\therefore V_o = -16.5 \text{ V}$$

Ans: The output will be -16.5 V .

10.9.

The given circuit resembles a summing circuit.

The output voltage is given as

$$V_o = - \left(\frac{R_f}{R_1} \times V_1 + \frac{R_f}{R_2} \times V_2 + \frac{R_f}{R_3} \times V_3 \right)$$

Given, $R_f = 68 \times 10^3 \Omega$

$$R_1 = 33 \times 10^3 \Omega$$

$$V_1 = 0.2 \text{ V}$$

$$R_2 = 22 \times 10^3 \Omega$$

$$V_2 = -0.5 \text{ V}$$

$$R_3 = 12 \times 10^3 \Omega$$

$$V_3 = 0.8 \text{ V}$$

$$\begin{aligned} \therefore V_o &= - \left(\frac{68 \times 10^3}{33 \times 10^3} \times 0.2 + \frac{68 \times 10^3}{22 \times 10^3} \times (-0.5) + \frac{68 \times 10^3}{12 \times 10^3} \times 0.8 \right) \\ &= - \left(\frac{68}{165} - \frac{17}{11} + \frac{68}{15} \right) \\ &= - \frac{17}{5} = -3.4 \end{aligned}$$

Ans: The output voltage is ~~$-\frac{17}{5} \text{ V}$~~
 -3.4 V .

10.11.

In the given OP amp, the input terminals have the same voltage. The output is short-circuited,

$$\therefore V_o = V_i$$

$$\Rightarrow V_o = 0.5 \text{ V} \quad [\because V_i = 0.5 \text{ V}]$$

Ans: The output voltage is 0.5 V

10.12.

For the first OP-amp the two terminals have same voltage, So, $V_o = V_i$

$$\therefore V_o = 1.5 \text{ V}$$

For the second OP-amp, it resembles an inverting amplifier. The formula is

$$V_o = -\left(\frac{R_f}{R_i}\right) \times V_i$$

$$\text{Given, } R_f = 100 \times 10^3 \Omega$$

$$R_i = 20 \times 10^3 \Omega \quad V_i = 1.5 \text{ V}$$

$$\therefore V_o = -\left(\frac{100 \times 10^3}{20 \times 10^3}\right) \times (1.5)$$

$$\therefore V_o = -7.5 \text{ V}$$

Ans: The output voltage is ~~7.5 V~~
-7.5 V.

10.13.

For the first OPamp, it resembles a unity follower.

The output voltage is $V_o = V_i$

$$\text{Given, } V_i = 0.2 \text{ V}$$

$$\therefore V_o = 0.2 \text{ V}$$

For the second OP amp, the configuration resembles an inverting amplifier. The output is

$$V_2 = -\frac{R_f}{R_i} \times V_i$$

$$\begin{aligned} \text{Given, } R_f &= 200 \times 10^3 \Omega \\ R_i &= 20 \times 10^3 \Omega \quad V_i = 0.2 \text{ V} \end{aligned}$$

$$\therefore V_2 = -\frac{200 \times 10^3}{20 \times 10^3} \times 0.2$$

$$\therefore V_2 = -2 \text{ V}$$

~~So,~~ Ans: The output voltage is -2 V .

For the third OP-amp, $V_3 = \left(1 + \frac{R_f}{R_i}\right) \times V_i$ [Non-inverting Amplifier]

$$= \left(1 + \frac{200 \times 10^3}{10 \times 10^3}\right) \times (0.2)$$

$$\therefore V_3 = 4.2 \text{ V}$$

Ans: 4.2 V

10.14.

The first OP amp resembles an inverting amplifier.

The output voltage is given as,

$$V_{o_1} = \left(1 + \frac{R_f}{R_i}\right) V_i$$

Given, $R_f = 400 \times 10^3 \Omega$

$R_i = 20 \times 10^3 \Omega$

$V_i = 0.1 \text{ V}$

$$\text{So, } V_{o_1} = \left(1 + \frac{400 \times 10^3}{20 \times 10^3}\right) (0.1)$$

$$= 2.1 \text{ V}$$

The second OP-amp resembles a unity follower.

The output voltage is

$$V_{o_2} = V_i$$

Given, $V_i = 0.1 \text{ V}$

$$\text{So, } V_{o_2} = 0.1 \text{ V}$$

For the third OP-amp, it resembles a summing amplifier.

The output formula is

$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right)$$

Given, $R_f = 100 \times 10^3 \Omega$

$R_1 = 20 \times 10^3 \Omega$

$R_2 = 10 \times 10^3 \Omega$

$V_1 = 2.1 \text{ V}$

$V_2 = 0.1 \text{ V}$

$$\therefore V_o = - \left(\frac{100 \times 10^3}{20 \times 10^3} \times 2.1 + \frac{100 \times 10^3}{10 \times 10^3} \times 0.1 \right)$$

$$= -11.5 \text{ V}$$

Ans: The output voltage is -11.5 V .

10.15.

The first OP amp is a summing amplifier.

The output is

$$V_o = - \left(\frac{R_f}{R_1} \times V_1 + \frac{R_f}{R_2} \times V_2 \right)$$

Given,

$$R_f = 600 \times 10^3 \Omega$$

$$R_1 = 15 \times 10^3 \Omega$$

$$R_2 = 30 \times 10^3 \Omega$$

$$V_1 = 0.025 \text{ V}$$

$$V_2 = -0.020 \text{ V}$$

$$V_{o_1} = - \left(\frac{600 \times 10^3}{15 \times 10^3} \times 0.025 + \frac{600 \times 10^3}{30 \times 10^3} \times (-0.02) \right)$$

$$= -600 \text{ mV}$$

Second OP amp resembles a unity follower.

$$\text{So, } V_{o_2} = V_2 = -20 \text{ mV}$$

The third OP-amp is also a summing amplifier.

Given,

$$R_f = 300 \times 10^3 \Omega$$

$$R_1 = 30 \times 10^3 \Omega$$

$$R_2 = 15 \times 10^3 \Omega$$

$$V_{o_1} = -0.6 \text{ V}$$

$$V_{o_2} = 0.02 \text{ V}$$

$$\therefore V_o = -\left(\frac{300 \times 10^3}{30 \times 10^3} \times (-0.6) + \frac{300 \times 10^3}{15 \times 10^3} \times (-0.02)\right)$$

$$\therefore V_o = -6.4 \text{ V}$$

Ans: The output voltage is -6.4 V .

10.23.

The logarithmic value of CMRR is

$$\text{CMRR} = 20 \log_{10} \frac{A_d}{A_c}$$

$$\text{Here, } A_d = \frac{V_o}{V_d} \text{ and } A_c = \frac{V_o}{V_c}$$

$$\text{Given, } V_o = 0.12 \text{ V}$$

$$V_d = 0.001 \text{ V} \quad \cancel{V_o}$$

$$\therefore A_d = \frac{0.12}{0.001} = 120 \text{ V}$$

$$\text{And, } A_c = V_o / V_c \text{ where, } V_o = 20 \times 10^{-6} \text{ V}$$

$$V_c = 0.001 \text{ V}$$

$$\therefore A_c \cancel{= 20 \times 10^{-6} / 0.001} = \frac{20 \times 10^{-6}}{0.001} = 0.02 \text{ V}$$

$$\text{So, CMRR} = 20 \log_{10} \frac{120}{0.02}$$

$$= 75.56 \text{ dB}$$

Ans: The value for CMRR is 75.56 dB .

10.24

(a) We know, $V_o = A_d V_d \left(1 + \frac{1}{CMRR} \times \frac{V_c}{V_d}\right)$

Here, $V_d = V_{i1} - V_{i2}$

$$= 200 \times 10^{-6} - 140 \times 10^{-6}$$

$$= 60 \times 10^{-6} \text{ V}$$

And, $V_c = \frac{V_{i1} + V_{i2}}{2} = \frac{200 \times 10^{-6} + 140 \times 10^{-6}}{2}$

$$= 170 \times 10^{-6} \text{ V}$$

Given, $CMRR = 200$

$$A_d = 6000$$

$$\therefore V_o = 6000 (60 \times 10^{-6}) \left(1 + \frac{1}{200} \times \frac{170 \times 10^{-6}}{60 \times 10^{-6}}\right)$$

$$\therefore V_o = 365.1 \times 10^{-3} \text{ V}$$

(b)

Again, putting $CMRR = 10^5$

$$V_o = 6000 \times (60 \times 10^{-6}) \times \left(1 + \frac{1}{10^5} \times \frac{170 \times 10^{-6}}{60 \times 10^{-6}}\right)$$

$$\therefore V_o = 360.01 \times 10^{-3} \text{ V}$$

Ans: ~~for (a) $V_o = 365.1 \text{ mV}$~~

for (a), output voltage is 365.1 mV

for (b), output voltage is 360.01 mV

11.1

The given circuit resembles an inverting amplifier.

$$V_o = -\frac{R_f}{R_i} \times V_i$$

$$\text{Given, } R_f = 180 \times 10^3 \Omega$$

$$R_i = 3600 \Omega = 3.6 \times 10^3 \Omega$$

$$V_i = 3.5 \times 10^{-3} \text{ V}_{\text{rms}}$$

$$\therefore V_o = -\frac{180 \times 10^3}{3.6 \times 10^3} \times 3.5 \times 10^{-3}$$

$$= -175 \text{ mV}_{\text{rms}}$$

Ans: The output voltage will be $-175 \text{ mV}_{\text{rms}}$.

11.2

The output voltage V_o for the given non-inverting amplifier is

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

$$\text{Given, } R_f = 750 \times 10^3 \Omega$$

$$R_i = 36 \times 10^3 \Omega$$

$$V_i = 150 \times 10^{-3} \text{ V}$$

$$\therefore V_o = \left(1 + \frac{750 \times 10^3}{36 \times 10^3}\right) \times (150 \times 10^{-3}) = 3.275 \text{ V}_{\text{rms}}$$

Ans: The output voltage will be $3.275 \text{ V}_{\text{rms}}$.

11.3

The first OPamp is in non-inverting mode and the next two are in inverting amplifier mode.

For non-inverting amplifier,

$$A_{V_1} = \left(1 + \frac{R_f}{R_i}\right) V_i$$

and for inverting amplifier,

$$A_{V_2} = \left(-\frac{R_f}{R_i}\right) \times V_i$$

So, the output voltage is

$$V_o = A_{V_1} \times A_{V_2} \times A_{V_3} \times V_i$$

$$= \left(1 + \frac{510 \times 10^3}{18 \times 10^3}\right) \left(-\frac{680 \times 10^3}{22 \times 10^3}\right) \left(-\frac{750 \times 10^3}{33 \times 10^3}\right) (20 \times 10^{-6})$$

$$= 412 \text{ mV}$$

Ans: The output voltage is 412 mV

11.6

The output voltage V_o of the summing amplifier is

$$V_o = - \left(\frac{R_f}{R_1} \times V_1 + \frac{R_f}{R_2} \times V_2 \right)$$

Given, $R_f = 4.7 \times 10^5 \Omega$

$$R_1 = 4.7 \times 10^4 \Omega$$

$$R_2 = 1.2 \times 10^4 \Omega$$

$$V_1 = 40 \times 10^{-3} \text{ V}$$

$$V_2 = 20 \times 10^{-3} \text{ V}$$

$$\begin{aligned} \therefore V_o &= - \left(\frac{4.7 \times 10^5}{4.7 \times 10^4} \times 40 \times 10^{-3} + \frac{4.7 \times 10^5}{1.2 \times 10^4} \times 20 \times 10^{-3} \right) \\ &= -1.18 \text{ V} \end{aligned}$$

Ans: The output voltage is -1.18 V .

11.7

The given circuit resembles a subtractor amplifier.

The output voltage is

$$\begin{aligned} V_o &= \frac{R_3}{R_1 + R_3} \times \frac{R_2 + R_4}{R_2} V_1 - \frac{R_4}{R_2} V_2 \\ &= \frac{10 \times 10^3}{10 \times 10^3 + 10 \times 10^3} \times \frac{150 \times 10^3 + 300 \times 10^3}{150 \times 10^3} \times 1 \\ &\quad - \frac{300 \times 10^3}{150 \times 10^3} \times 2 \\ &= 0.5 \times 3 \times 1 - 2 \times 2 \\ &= -2.5 \text{ V} \end{aligned}$$

Ans: The output voltage is -2.5 V

~~10.8~~ 11.8

The given circuit resembles a subtractor amplifier.
The output voltage is

$$V_o = -\left(\frac{R_f}{R_3} \left(-\frac{R_f}{R_1} \times V_1\right) + \frac{R_f}{R_2} V_2\right)$$

Given, $R_f = 3.3 \times 10^5 \Omega$

$$R_3 = 3.3 \times 10^4 \Omega$$

$$V_1 = 12 \times 10^{-3} \text{ V}$$

$$R_2 = 4.7 \times 10^4 \Omega$$

$$V_2 = 18 \times 10^{-3} \text{ V}$$

$$R_1 = 4.7 \times 10^4 \Omega$$

$$\therefore V_o = -\left[\frac{3.3 \times 10^5}{3.3 \times 10^4} \times (12 \times 10^{-3}) \left(\frac{4.7 \times 10^5}{4.7 \times 10^4}\right) + \frac{4.7 \times 10^5}{4.7 \times 10^4} (18 \times 10^{-3})\right]$$

$$= -[-1.2 + 0.18]$$

$$= 1.02 \text{ V}$$

Ans:

So, the output voltage is 1.02 V.

11.13

The output current can be written as

$$V_o = -\frac{R_F}{R_i} \times V_i \quad [\text{For inverting amplifier}]$$

$$\Rightarrow I_o = \frac{R_F}{R_i} \times V_i \left(\frac{1}{R_o} \right) \quad [\because V_o = I_o R_o]$$

Given, $R_F = 100 \times 10^3 \Omega$

$R_i = 200 \times 10^3 \Omega$

$R_o = 10 \Omega$

$V_i = 10 \times 10^{-3} \text{ V}$

$$\therefore I_o = \frac{100 \times 10^3}{200 \times 10^3} \times \frac{1}{10} \times 10 \times 10^{-3}$$

$$= 0.5 \text{ mA}$$

Ans: The output current is 0.5 mA

11.14

The output voltage for the amplifier is

$$V_o = \left(1 + \frac{2R}{R_p} \right) (V_2 - V_1)$$

Given, $R = 5000 \Omega$ $V_2 = 1 \text{ V}$

$R_p = 1000 \Omega$ $V_1 = 3 \text{ V}$

$$\therefore V_o = \left(1 + \frac{2 \times 5000}{1000} \right) (1 - 3)$$

$$= -22 \text{ V}$$

Ans: The output voltage is -22V.