

# Instrumental Amplification


Name - Md Farhan Ghuman

Dept - Computer Science and Engineering

Section - CSE A

ID: - 180041120

Date - 13 - October - 2020

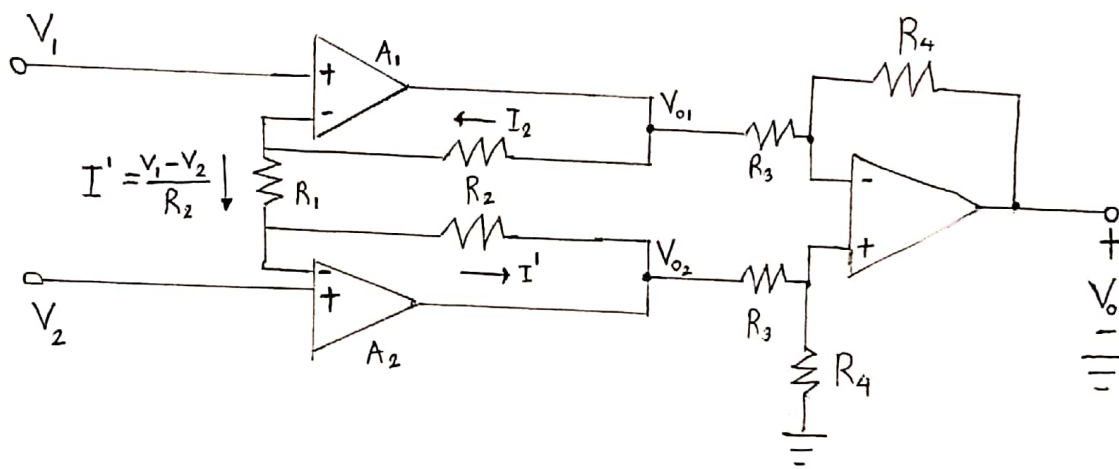

The given diagram shows the circuit design of an instrumental amplifier.

A<sub>1</sub> is an inverting amplifier

A<sub>2</sub> is a non-inverting amplifier.

A<sub>3</sub> is a difference amplifier.

For the difference amplifier,  $A_3$

$$\begin{aligned}
 V_o &= V_{o1} - V_{o2} \quad \left| \quad \begin{aligned} V_{o1} &= \frac{V_1 - V_2}{R_1} \times R_2 + V \\ V_{o2} &= V_2 - \frac{V - V_2}{R_1} R_2 \end{aligned} \right. \\
 &= \frac{(V_1 - V_2)}{R_1} R_2 + (V_1 - V_2) + \frac{(V_1 - V_2)}{R_1} R_2 \\
 &= (V_1 - V_2) \left( \frac{R_2}{R_1} + 1 + \frac{R_2}{R_1} \right) \\
 &= (V_1 - V_2) \left( 1 + \frac{2R_2}{R_1} \right)
 \end{aligned}$$

For the inverting amplifier,  $A_1$ ,

$$\begin{aligned}
 V_{out} &= - \frac{R_f}{R_{in}} \times V_{in} \\
 \Rightarrow V_{o1} &= -V_{o2} \left[ \frac{R_4}{R_3} \right]
 \end{aligned}$$

For non-inverting amplifier,  $A_2$ ,

$$\begin{aligned}
 V_{out} &= V_{in} \left( \frac{R_{in} + R_f}{R_{in}} \right) \\
 \Rightarrow V_{o2} &= V_{o1} \left[ \frac{R_4}{R_3 + R_4} \right] \left[ 1 + \frac{R_4}{R_3} \right]
 \end{aligned}$$

So, difference amplifier,  $A_3$  [sum of outputs produced by each input]

$$\begin{aligned}
 V_{out} &= V_{o1} + V_{o2} = V_{o2} \left[ \frac{R_4}{R_3 + R_4} \right] \left[ 1 + \frac{R_4}{R_3} \right] - V_{o1} \left[ \frac{R_4}{R_3} \right] \\
 &= V_{o2} \left[ \frac{R_4}{R_3 + R_4} \right] \left[ \frac{R_3}{R_3} + \frac{R_4}{R_3} \right] - V_{o1} \left[ \frac{R_4}{R_3} \right] \\
 &= V_{o2} \left[ \frac{R_4}{R_3 + R_4} \right] \left[ \frac{R_3 + R_4}{R_3} \right] - V_{o1} \left[ \frac{R_4}{R_3} \right]
 \end{aligned}$$

(2)

$$\begin{aligned}
&= V_{o2} \left[ \frac{R_4}{R_3} \right] - V_{o1} \left[ \frac{R_4}{R_3} \right] \\
&= (V_{o2} - V_{o1}) \left[ \frac{R_4}{R_3} \right] \\
&= -(V_1 - V_2) \left[ 1 + \frac{R_2}{R_1} \right] \left[ \frac{R_4}{R_3} \right] \\
&= (V_2 - V_1) \left[ 1 + \frac{R_2}{R_1} \right] \times \left[ \frac{R_4}{R_3} \right]
\end{aligned}$$

For  $R_2 = R_3 = R_4$

$$V_{out} = (V_2 - V_1) \left[ 1 + \frac{R_2}{R_1} \right]$$