

EEE 4484

Lab 05

Submitted by:

Sidratul Muntaha
CSE-A

Std_ID: 180041118

TASK 01: FULL ADDER

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity full_adder is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        Cin : in STD_LOGIC;
        S : out STD_LOGIC;
        Cout : out STD_LOGIC);
end full_adder;

architecture gate_level of full_adder is

begin

  S <= A XOR B XOR Cin ;
  Cout <= (A AND B) OR (Cin AND A) OR (Cin AND B)

; end gate_level;
```

TESTBENCH Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_full_adder IS
END tb_full_adder;

ARCHITECTURE behavior OF tb_full_adder IS

  --Component Declaration for the Unit Under Test (UUT)

  COMPONENT full_adder
  PORT (
    A : IN std_logic;
    B : IN std_logic;
```

```

Cin : IN std_logic;
S : OUT std_logic;
Cout : OUT
std_logic );
END COMPONENT;

--Inputs
signal A : std_logic := '0';
signal B : std_logic := '0';
signal Cin : std_logic := '0';

--Outputs
signal S : std_logic;
signal Cout : std_logic;

BEGIN

--Instantiate the Unit Under Test (UUT)
uut: full_adder PORT MAP (
A=>A,
B=>B,
Cin => Cin,
S=>S,
Cout => Cout
);

--Stimulus process
stim_proc: process
begin
--hold reset state for 100 ns.
Wait for 100 ns;

--insert stimulus here
A <= '1';
B <= '0';
Cin <= '0';
wait for 10 ns;

A <= '0';
B <= '1';
Cin <= '0';
wait for 10 ns;

A <= '1';
B <= '1';
Cin <= '0';
wait for 10 ns;

A <= '0';
B <= '0';
Cin <= '1';
wait for 10 ns;

```

```

A <= '1';
B <= '0';
Cin <= '1';
wait for 10 ns;

A <= '0';
B <= '1';
Cin <= '1';
wait for 10 ns;


A <= '1';
B <= '1';
Cin <= '1';
wait for 10 ns;

end process;

END;

```

OUTPUT

 

TASK 02: 1 TO 8 DEMULTIPLEXER

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity demux_1x8 is
port (
    i:in std_logic;
    s:in std_logic_vector(2 downto 0);
    o:out std_logic_vector(7 downto 0)
);
end demux_1x8;

architecture behavioral of demux_1x8
is begin
    o(0) <= i when s="000" else '0';
    o(1) <= i when s="001" else '0';
    o(2) <= i when s="010" else '0';
    o(3) <= i when s="011" else '0';
    o(4) <= i when s="100" else '0';
    o(5) <= i when s="101" else '0';
    o(6) <= i when s="110" else '0';
    o(7) <= i when s="111" else '0';
end behavioral;
```

TESTBENCH Code

```
library ieee;
use ieee.std_logic_1164.all;

entity tb_demux_1x8 is
end tb_demux_1x8;

architecture behavioral of tb_demux_1x8 is

component demux_1x8
port (
    i:in std_logic;
    s:in std_logic_vector(2 downto 0);
    o:out std_logic_vector(7 downto 0)
);
end component;

-- Inputs
```

```

signal tb_i : std_logic := '0';
signal tb_s : std_logic_vector (2 downto 0) := (others => '0');

-- Outputs
signal tb_o : std_logic_vector (7 downto 0) := (others => '0');

begin

uut: demux_1x8 port map (
    i => tb_i,
    s => tb_s,
    o => tb_o
);

-- stimulus process
stim_process:
process begin
    tb_i<='1';
    wait for 10 ns;
    tb_s <= "000";
    wait for 10 ns;
    tb_s <= "001";
    wait for 10 ns;
    tb_s <= "010";
    wait for 10 ns;
    tb_s <= "011";
    wait for 10 ns;
    tb_s <= "100";
    wait for 10 ns;
    tb_s <= "101";
    wait for 10 ns;
    tb_s <= "110";
    wait for 10 ns;
    tb_s <= "111";
    wait for 20 ns;
    tb_i<='0'; wait
    for 10 ns; tb_s
    <= "000"; wait
    for 10 ns; tb_s
    <= "001"; wait
    for 10 ns; tb_s
    <= "010"; wait
    for 10 ns; tb_s
    <= "011"; wait
    for 10 ns; tb_s
    <= "100"; wait
    for 10 ns; tb_s
    <= "101"; wait
    for 10 ns; tb_s
    <= "110"; wait
    for 10 ns; tb_s
    <= "111";

```


```

        wait for 20 ns;
end process;

end architecture behavioral;

```

OUTPUT

 

TASK 03: 4 BIT ALU

VHDL Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

entity alu_op is
  Port (
    inp_a : in signed(3 downto 0);
    inp_b : in signed(3 downto 0);
    sel : in STD_LOGIC_VECTOR (2 downto 0);
    out_alu : out signed(3 downto 0));
end alu_op;

architecture Behavioral of alu_op is
begin
  process(inp_a, inp_b, sel)
  begin
    case sel is
      when "000" =>
        out_alu<= inp_a + inp_b; --addition
      when "001" =>
        out_alu<= inp_a - inp_b; --subtraction
      when "010" =>
        out_alu<= inp_a - 1; --sub 1
      when "011" =>
        out_alu<= inp_a + 1; --add 1
      when "100" =>
        out_alu<= inp_a and inp_b; -- AND gate
      when "101" =>
        out_alu<= inp_a or inp_b; --OR gate
      when "110" =>
        out_alu<= not inp_a ; --NOT gate
      when "111" =>
        out_alu<= inp_a xor inp_b; --XOR gate
      when others =>
        NULL;
    end case;
  end process;

end Behavioral;
```


TESTBENCH Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_alu_op IS
END tb_alu_op;

ARCHITECTURE behavior OF tb_alu_op IS

    --Component Declaration for the Unit Under Test (UUT)

    COMPONENT alu_op
    PORT(
        inp_a : IN signed(3 downto 0);
        inp_b : IN signed(3 downto 0);
        sel : IN std_logic_vector(2 downto 0);
        out_alu : OUT signed(3 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal inp_a : signed(3 downto 0) := (others => '0');
    signal inp_b : signed(3 downto 0) := (others => '0');
    signal sel : std_logic_vector(2 downto 0) := (others => '0');

    -- Outputs
    signal out_alu : signed(3 downto 0);

BEGIN

    --Instantiate the Unit Under Test (UUT)
    uut: alu_op PORT MAP (
        inp_a => inp_a,
        inp_b => inp_b,
        sel => sel,
        out_alu => out_alu
    );

    --Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.

        Wait for 100 ns;
```


```
-- insert stimulus here
```

```
inp_a <= "1001";  
inp_b <= "1111";
```

```
sel <= "000";  
wait for 100 ns;  
sel <= "001";  
wait for 100 ns;  
sel <= "010";  
wait for 100 ns;  
sel <= "011";  
wait for 100 ns;  
sel <= "100";  
wait for 100 ns;  
sel <= "101";  
wait for 100 ns;  
sel <= "110";  
wait for 100 ns;  
sel <= "111";  
end process;
```

```
END;
```

OUTPUT

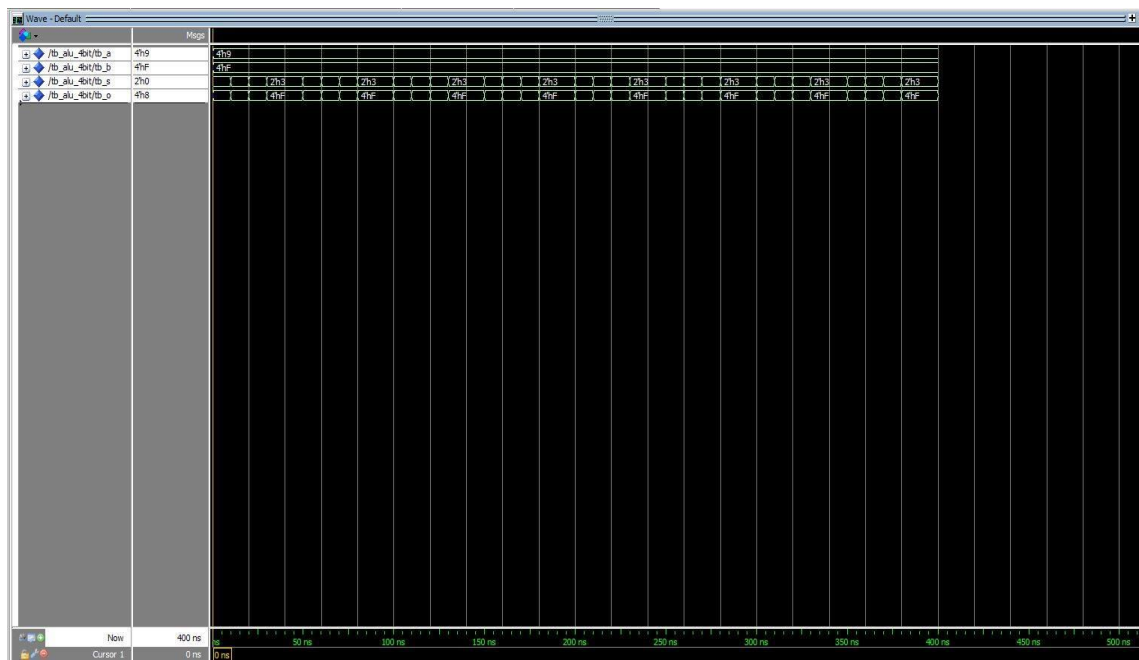

TASK 04: 5-BIT SHIFT REGISTER

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shift_reg_5bit is
port(
    clk : in std_logic;
    D: in std_logic_vector(3 downto 0);
    Q: out std_logic_vector(3 downto 0)
);
end shift_reg_5bit;

architecture behavioral of shift_reg_5bit is

begin
process (clk,D)
begin
    if (clk'event and clk='1') then Q <=
        D; end if;
end process;

end behavioral;
```

TESTBENCH Code

```
library ieee;
use ieee.std_logic_1164.all;

entity tb_shift_reg_5bit is
end tb_shift_reg_5bit;

architecture behavioral of tb_shift_reg_5bit is

component shift_reg_5bit
port(
    clk : in std_logic;
    D : in std_logic_vector(3 downto 0);
    Q : out std_logic_vector(3 downto 0)
);
end component;

signal tb_clk : std_logic;
signal tb_D : std_logic_vector(3 downto 0);
signal tb_Q : std_logic_vector(3 downto 0);
constant clk_period : time := 100 ns;
```

```

begin
    uut: shift_reg_5bit port map(
        clk => tb_clk,
        D => tb_D,
        Q => tb_Q
    );

    -- clock process

clk_process: process
begin
    tb_clk <= '0';
    wait for clk_period/2;
    tb_clk <= '1';
    wait for clk_period/2;
end process;

-- stimulus process
stim_process:
process begin
    tb_D<="0000";
    wait for 100 ns;
    tb_D <= "0100";
    wait for 100 ns;
    tb_D <= "1010";
    wait for 100 ns;
    tb_D <= "0110";
    wait for 100 ns;
end process;

end architecture behavioral;

```

OUTPUT

