

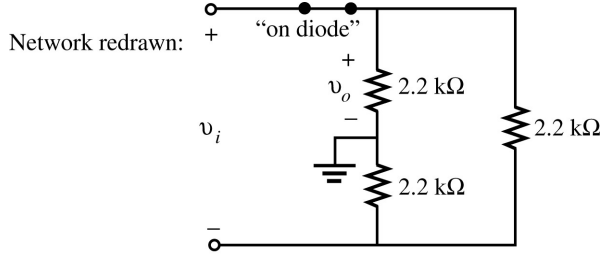


30. Positive half-cycle of  $v_i$ :

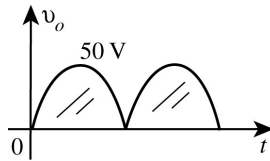

Negative half-cycle of  $v_i$ :

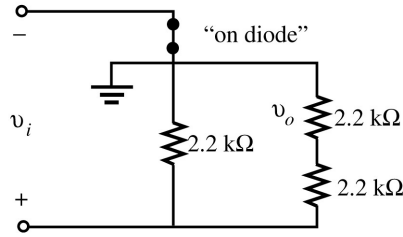

$$V_{dc} = 0.636V_m = 0.636(50 \text{ V}) = 31.8 \text{ V}$$

Voltage-divider rule:

$$\begin{aligned} V_{o_{\max}} &= \frac{2.2 \text{ k}\Omega(V_{i_{\max}})}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} \\ &= \frac{1}{2}(V_{i_{\max}}) \\ &= \frac{1}{2}(100 \text{ V}) \\ &= 50 \text{ V} \end{aligned}$$

Polarity of  $v_o$  across the  $2.2 \text{ k}\Omega$  resistor acting as a load is the same.

Voltage-divider rule:

$$\begin{aligned} V_{o_{\max}} &= \frac{2.2 \text{ k}\Omega(V_{i_{\max}})}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} \\ &= \frac{1}{2}(V_{i_{\max}}) \\ &= \frac{1}{2}(100 \text{ V}) \\ &= 50 \text{ V} \end{aligned}$$

31. Positive pulse of  $v_i$ :

Top left diode "off", bottom left diode "on"

$$2.2 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega = 1.1 \text{ k}\Omega$$

$$V_{o_{\text{peak}}} = \frac{1.1 \text{ k}\Omega(170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$

Negative pulse of  $v_i$ :

Top left diode "on", bottom left diode "off"

$$V_{o_{\text{peak}}} = \frac{1.1 \text{ k}\Omega(170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$


$$V_{dc} = 0.636(56.67 \text{ V}) = 36.04 \text{ V}$$

32. (a) Si diode open for positive pulse of  $v_i$  and  $v_o = 0 \text{ V}$

For  $-20 \text{ V} < v_i \leq -0.7 \text{ V}$  diode "on" and  $v_o = v_i + 0.7 \text{ V}$ .

$$\text{For } v_i = -20 \text{ V}, v_o = -20 \text{ V} + 0.7 \text{ V} = -19.3 \text{ V}$$
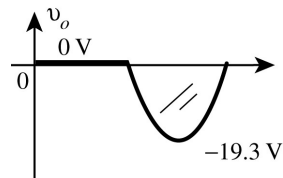
$$\text{For } v_i = -0.7 \text{ V}, v_o = -0.7 \text{ V} + 0.7 \text{ V} = 0 \text{ V}$$



- (b) For  $v_i \leq 8 \text{ V}$  the 8 V battery will ensure the diode is forward-biased and  $v_o = v_i - 8 \text{ V}$ .


At  $v_i = 8 \text{ V}$

$$v_o = 8 \text{ V} - 8 \text{ V} = \mathbf{0 \text{ V}}$$

At  $v_i = -20 \text{ V}$

$$v_o = -20 \text{ V} - 8 \text{ V} = \mathbf{-28 \text{ V}}$$

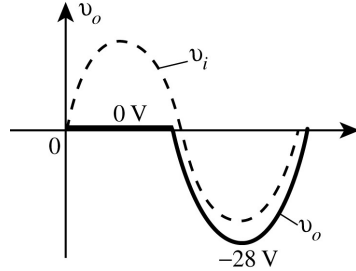For  $v_i > 8 \text{ V}$  the diode is reverse-biased and  $v_o = \mathbf{0 \text{ V}}$ .




33. (a) Positive pulse of  $v_i$ :

$$V_o = \frac{1.8 \text{ k}\Omega(12 \text{ V} - 0.7 \text{ V})}{1.8 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \mathbf{5.09 \text{ V}}$$

Negative pulse of  $v_i$ :

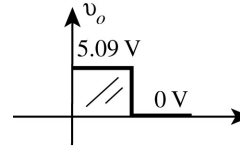diode "open",  $v_o = \mathbf{0 \text{ V}}$




- (b) Positive pulse of  $v_i$ :

$$V_o = 12 \text{ V} - 0.7 \text{ V} + 4 \text{ V} = \mathbf{15.3 \text{ V}}$$

Negative pulse of  $v_i$ :

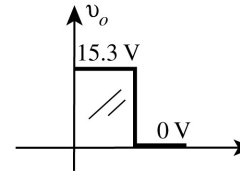diode "open",  $v_o = \mathbf{0 \text{ V}}$




34. (a) For  $v_i = 20 \text{ V}$  the diode is reverse-biased and  $v_o = \mathbf{0 \text{ V}}$ .

For  $v_i = -5 \text{ V}$ ,  $v_i$  overpowers the 4 V battery and the diode is "on".

Applying Kirchhoff's voltage law in the clockwise direction:

$$-5 \text{ V} + 4 \text{ V} - v_o = 0$$

$$v_o = \mathbf{-1 \text{ V}}$$

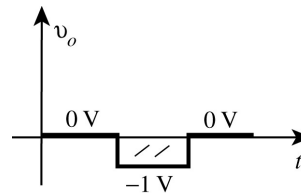


- (b) For  $v_i = 20 \text{ V}$  the 20 V level overpowers the 5 V supply and the diode is "on". Using the short-circuit equivalent for the diode we find  $v_o = v_i = \mathbf{20 \text{ V}}$ .


For  $v_i = -5 \text{ V}$ , both  $v_i$  and the 5 V supply reverse-bias the diode and separate  $v_i$  from  $v_o$ .

However,  $v_o$  is connected directly through the 2.2 k $\Omega$  resistor to the 5 V supply and

$v_o = \mathbf{5 \text{ V}}$ .

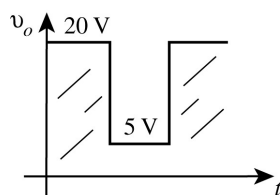

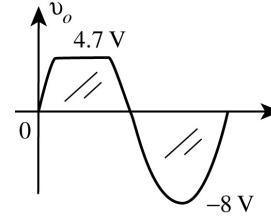35. (a) Diode “on” for  $v_i \geq 4.7 \text{ V}$   
 For  $v_i > 4.7 \text{ V}$ ,  $V_o = 4 \text{ V} + 0.7 \text{ V} = \mathbf{4.7 \text{ V}}$   
 For  $v_i < 4.7 \text{ V}$ , diode “off” and  $v_o = v_i$




- (b) Again, diode “on” for  $v_i \geq 3.7 \text{ V}$  but  $v_o$  now defined as the voltage across the diode  
 For  $v_i \geq 3.7 \text{ V}$ ,  $v_o = \mathbf{0.7 \text{ V}}$

For  $v_i < 3.7 \text{ V}$ , diode “off”,  $I_D = I_R = 0 \text{ mA}$  and  $V_{2.2 \text{ k}\Omega} = IR = (0 \text{ mA})R = 0 \text{ V}$

Therefore,  $v_o = v_i - 3 \text{ V}$

At  $v_i = 0 \text{ V}$ ,  $v_o = \mathbf{-3 \text{ V}}$

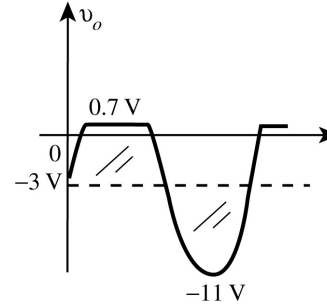$v_i = -8 \text{ V}$ ,  $v_o = -8 \text{ V} - 3 \text{ V} = \mathbf{-11 \text{ V}}$



36. For the positive region of  $v_i$ :  
 The right Si diode is reverse-biased.  
 The left Si diode is “on” for levels of  $v_i$  greater than  $5.3 \text{ V} + 0.7 \text{ V} = 6 \text{ V}$ . In fact,  $v_o = \mathbf{6 \text{ V}}$  for  $v_i \geq 6 \text{ V}$ .


For  $v_i < 6 \text{ V}$  both diodes are reverse-biased and  $v_o = v_i$ .

For the negative region of  $v_i$ :

The left Si diode is reverse-biased.

The right Si diode is “on” for levels of  $v_i$  more negative than  $7.3 \text{ V} + 0.7 \text{ V} = 8 \text{ V}$ . In fact,  $v_o = \mathbf{-8 \text{ V}}$  for  $v_i \leq -8 \text{ V}$ .

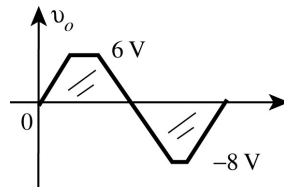For  $v_i > -8 \text{ V}$  both diodes are reverse-biased and  $v_o = v_i$ .



$i_R$ : For  $-8 \text{ V} < v_i < 6 \text{ V}$  there is no conduction through the  $10 \text{ k}\Omega$  resistor due to the lack of a complete circuit. Therefore,  $i_R = 0 \text{ mA}$ .

For  $v_i \geq 6 \text{ V}$

$$v_R = v_i - v_o = v_i - 6 \text{ V}$$

For  $v_i = 10 \text{ V}$ ,  $v_R = 10 \text{ V} - 6 \text{ V} = 4 \text{ V}$

$$\text{and } i_R = \frac{4 \text{ V}}{10 \text{ k}\Omega} = \mathbf{0.4 \text{ mA}}$$


For  $v_i \leq -8 \text{ V}$

$$v_R = v_i - v_o = v_i + 8 \text{ V}$$


For  $v_i = -10 \text{ V}$

$$v_R = -10 \text{ V} + 8 \text{ V} = -2 \text{ V}$$
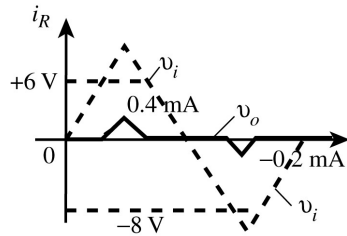
$$\text{and } i_R = \frac{-2 \text{ V}}{10 \text{ k}\Omega} = -0.2 \text{ mA}$$




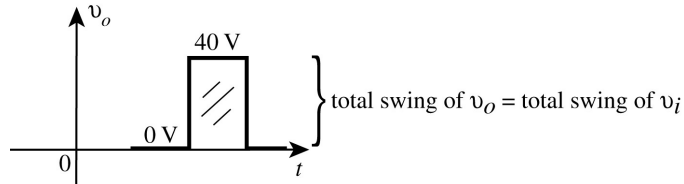37. (a) Starting with  $v_i = -20 \text{ V}$ , the diode is in the “on” state and the capacitor quickly charges to  $-20 \text{ V}+$ . During this interval of time  $v_o$  is across the “on” diode (short-current equivalent) and  $v_o = 0 \text{ V}$ .  
When  $v_i$  switches to the  $+20 \text{ V}$  level the diode enters the “off” state (open-circuit equivalent) and  $v_o = v_i + v_C = 20 \text{ V} + 20 \text{ V} = +40 \text{ V}$




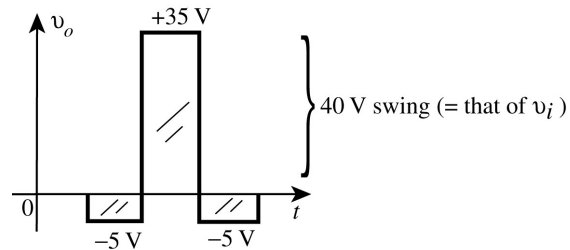- (b) Starting with  $v_i = -20 \text{ V}$ , the diode is in the “on” state and the capacitor quickly charges up to  $-15 \text{ V}+$ . Note that  $v_i = +20 \text{ V}$  and the  $5 \text{ V}$  supply are additive across the capacitor. During this time interval  $v_o$  is across “on” diode and  $5 \text{ V}$  supply and  $v_o = -5 \text{ V}$ .


When  $v_i$  switches to the  $+20 \text{ V}$  level the diode enters the “off” state and  $v_o = v_i + v_C = 20 \text{ V} + 15 \text{ V} = 35 \text{ V}$ .




38. (a) For negative half cycle capacitor charges to peak value of  $120\text{ V} = 120\text{ V}$  with polarity  $(- \text{---} | \text{---} +)$ . The output  $v_o$  is directly across the “on” diode resulting in  $v_o = \mathbf{0\text{ V}}$  as a negative peak value.  
For next positive half cycle  $v_o = v_i + 120\text{ V}$  with peak value of  $v_o = 120\text{ V} + 120\text{ V} = \mathbf{240\text{ V}}$ .

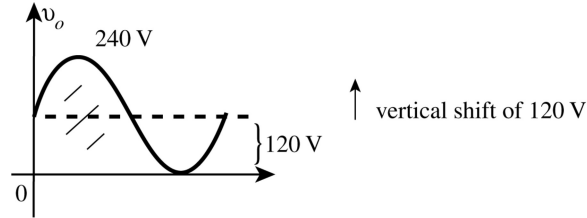

- (b) For positive half cycle capacitor charges to peak value of  $120\text{ V} - 20\text{ V} = 100\text{ V}$  with polarity  $(+ \text{---} | \text{---} -)$ . The output  $v_o = 20\text{ V} = \mathbf{20\text{ V}}$   
For next negative half cycle  $v_o = v_i - 100\text{ V}$  with negative peak value of  $v_o = -120\text{ V} - 100\text{ V} = \mathbf{-220\text{ V}}$ .

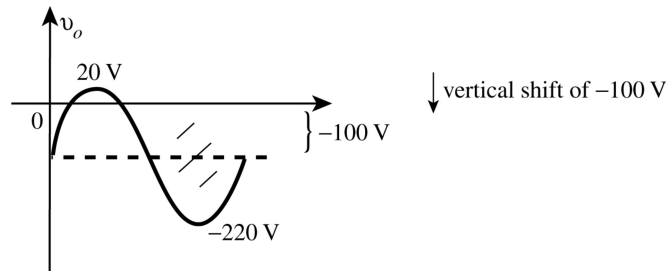


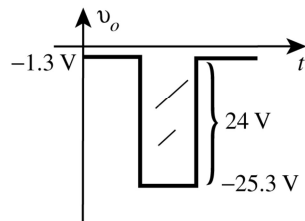39. (a)  $\tau = RC = (56\text{ k}\Omega)(0.1\text{ }\mu\text{F}) = 5.6\text{ ms}$   
 $5\tau = \mathbf{28\text{ ms}}$
- (b)  $5\tau = 28\text{ ms} \gg \frac{T}{2} = \frac{1\text{ ms}}{2} = \mathbf{0.5\text{ ms}}, 56:1$
- (c) Positive pulse of  $v_i$ :  
Diode “on” and  $v_o = -2\text{ V} + 0.7\text{ V} = -1.3\text{ V}$   
Capacitor charges to  $12\text{ V} + 2\text{ V} - 0.7\text{ V} = 13.3\text{ V}$
- Negative pulse of  $v_i$ :  
Diode “off” and  $v_o = -12\text{ V} - 13.3\text{ V} = -25.3\text{ V}$



40. Solution is network of Fig. 2.181(b) using a 10 V supply in place of the 5 V source.

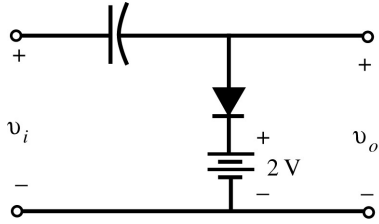41. Network of Fig. 2.178 with 2 V battery reversed.



42. (a) In the absence of the Zener diode

$$V_L = \frac{180 \Omega (20 \text{ V})}{180 \Omega + 220 \Omega} = 9 \text{ V}$$

$$V_L = 9 \text{ V} < V_Z = 10 \text{ V} \text{ and diode non-conducting}$$

$$\text{Therefore, } I_L = I_R = \frac{20 \text{ V}}{220 \Omega + 180 \Omega} = \mathbf{50 \text{ mA}}$$

$$\text{with } I_Z = \mathbf{0 \text{ mA}}$$

$$\text{and } V_L = \mathbf{9 \text{ V}}$$

- (b) In the absence of the Zener diode

$$V_L = \frac{470 \Omega (20 \text{ V})}{470 \Omega + 220 \Omega} = 13.62 \text{ V}$$

$$V_L = 13.62 \text{ V} > V_Z = 10 \text{ V} \text{ and Zener diode "on"}$$

$$\text{Therefore, } V_L = \mathbf{10 \text{ V}} \text{ and } V_{R_s} = 10 \text{ V}$$

$$I_{R_s} = V_{R_s} / R_s = 10 \text{ V} / 220 \Omega = \mathbf{45.45 \text{ mA}}$$

$$I_L = V_L / R_L = 10 \text{ V} / 470 \Omega = \mathbf{21.28 \text{ mA}}$$

$$\text{and } I_Z = I_{R_s} - I_L = 45.45 \text{ mA} - 21.28 \text{ mA} = \mathbf{24.17 \text{ mA}}$$

- (c)  $P_{Z_{\max}} = 400 \text{ mW} = V_Z I_Z = (10 \text{ V})(I_Z)$

$$I_Z = \frac{400 \text{ mW}}{10 \text{ V}} = 40 \text{ mA}$$

$$I_{L_{\min}} = I_{R_s} - I_{Z_{\max}} = 45.45 \text{ mA} - 40 \text{ mA} = 5.45 \text{ mA}$$

$$R_L = \frac{V_L}{I_{L_{\min}}} = \frac{10 \text{ V}}{5.45 \text{ mA}} = \mathbf{1,834.86 \Omega}$$

Large  $R_L$  reduces  $I_L$  and forces more of  $I_{R_s}$  to pass through Zener diode.

- (d) In the absence of the Zener diode

$$V_L = 10 \text{ V} = \frac{R_L (20 \text{ V})}{R_L + 220 \Omega}$$

$$10R_L + 2200 = 20R_L$$

$$10R_L = 2200$$

$$R_L = \mathbf{220 \Omega}$$