




Islamic University of Technology

EEE 4483


Digital Electronics & Pulse Techniques

Lecture- 4

Bi-stable Multivibrator using Op-Amp

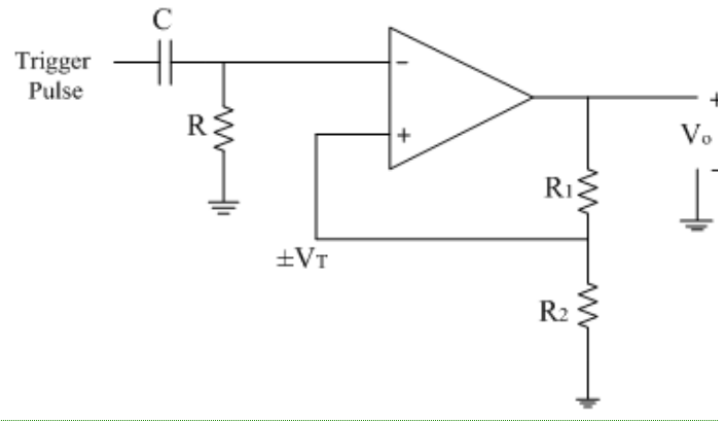

In this circuit, both the states at the output ($+V_{sat}$ and $-V_{sat}$) are stable states. *i.e.* the circuit remains in the same state till the external input is applied. If we want to change the output state a triggering pulse is applied. Now the state obtained after the pulse is applied is a permanent stable state. If we want to change the state again, we have to apply a triggering pulse. Thus by only application of trigger pulse, output changes its state. Thus to get the original state back, two triggering pulses need to be applied.

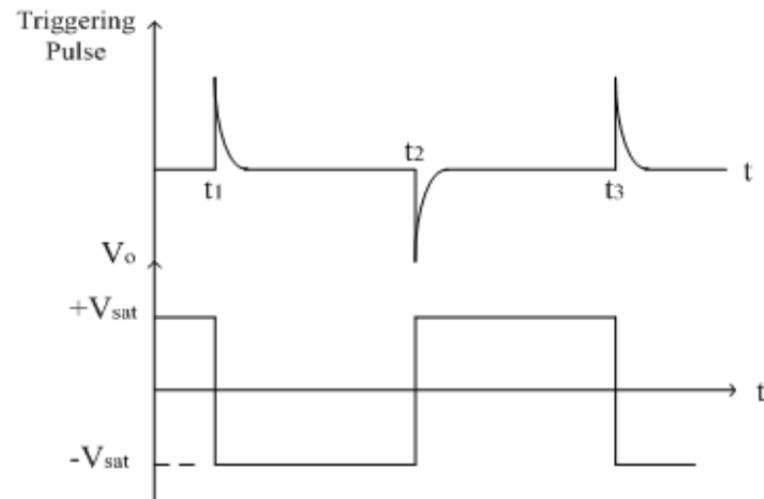


Duty Cycle

In general terms duty cycle means proportion of time for which device is operated. In terms of square wave signal it defines the percentage of time for which signal is at logic high level. For square wave it can be calculated as (high time / (high time + low time))

Duty cycle is the ratio of time a load or circuit is **ON** compared to the time the load or circuit is **OFF**.

Duty cycle, sometimes called “duty factor,” is expressed as a percentage of **ON** time. A 60% duty cycle is a signal that is **ON** 60% of the time and **OFF** the other 40%

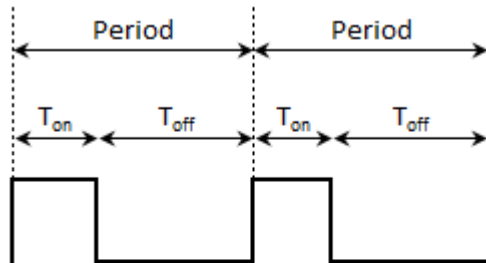Duty cycle of 50% means that the low time and high time of the signal is same.



$$\text{Period} = 1 / \text{Frequency}$$

$$\text{Period} = T_{\text{on}} + T_{\text{off}}$$

$$\text{Duty Cycle} = T_{\text{on}} / (T_{\text{on}} + T_{\text{off}}) * 100$$

(On Percentage)

50% duty cycle



75% duty cycle




25% duty cycle



555: A Versatile Device

- The 555 Timer is one of the best known IC's.
 - The 555 is part of every experimenter's tool kit
- Capable of creating a wide variety of circuits, including:
 - Oscillators with adjustable frequency and Duty Cycle
 - Monostable Multivibrators
 - Analog to digital Converters
 - Frequency Meters
 - Many other applications....

Capacitor Charge Cycle

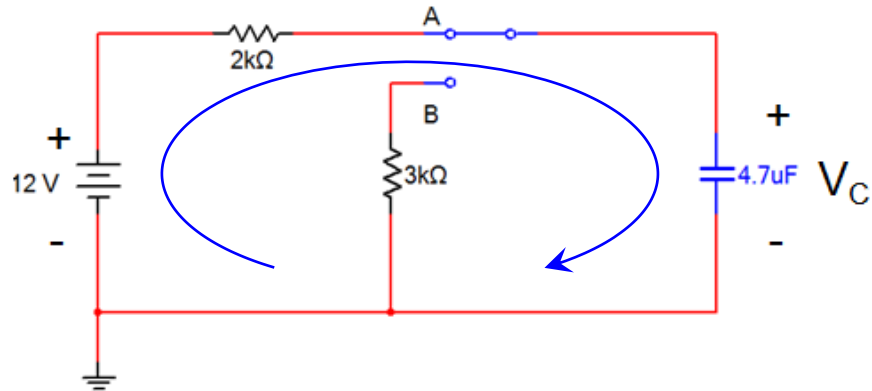

- Capacitor is initially discharged.
- Switch is moved to position A.
- Capacitor will charge to +12 v.
- Capacitor will charge through the 2 K Ω resistor.

Equation for Charging Capacitor

$$V_C = (V_{\text{Final}} - V_{\text{Initial}}) \times (1 - e^{-t/RC}) + V_{\text{Initial}}$$


Where :

V_C = The voltage across the capacitor

V_{Final} = The voltage across the capacitor that is fully charged

V_{Initial} = Any initial voltage across the capacitor as it begins to charge

Capacitor Discharge Cycle

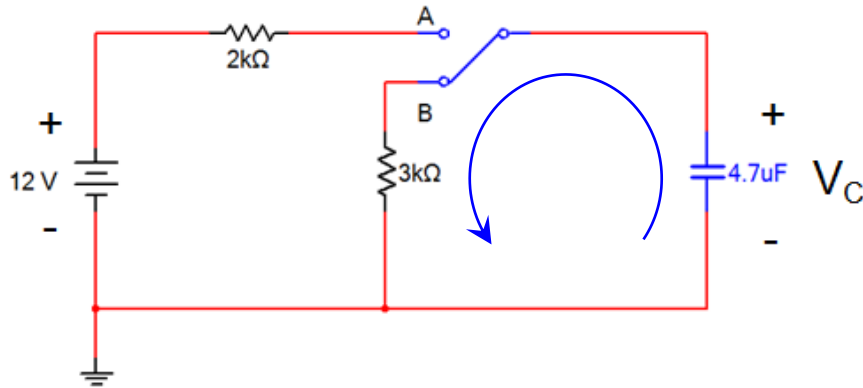

- Capacitor is initially charged.
- Switch is moved to position B.
- Capacitor will discharge to +0 v.
- Capacitor will discharge through the 3 KΩ resistor.

Equation for Discharging Capacitor

$$V_C = (V_{\text{Initial}} - V_{\text{Final}}) \times (e^{-t/RC})$$



Where :

V_C = The voltage across the capacitor

V_{Final} = The voltage across the capacitor that is fully discharged

V_{Initial} = Any initial voltage across the capacitor as it begins to discharge

Capacitor Charge & Discharge

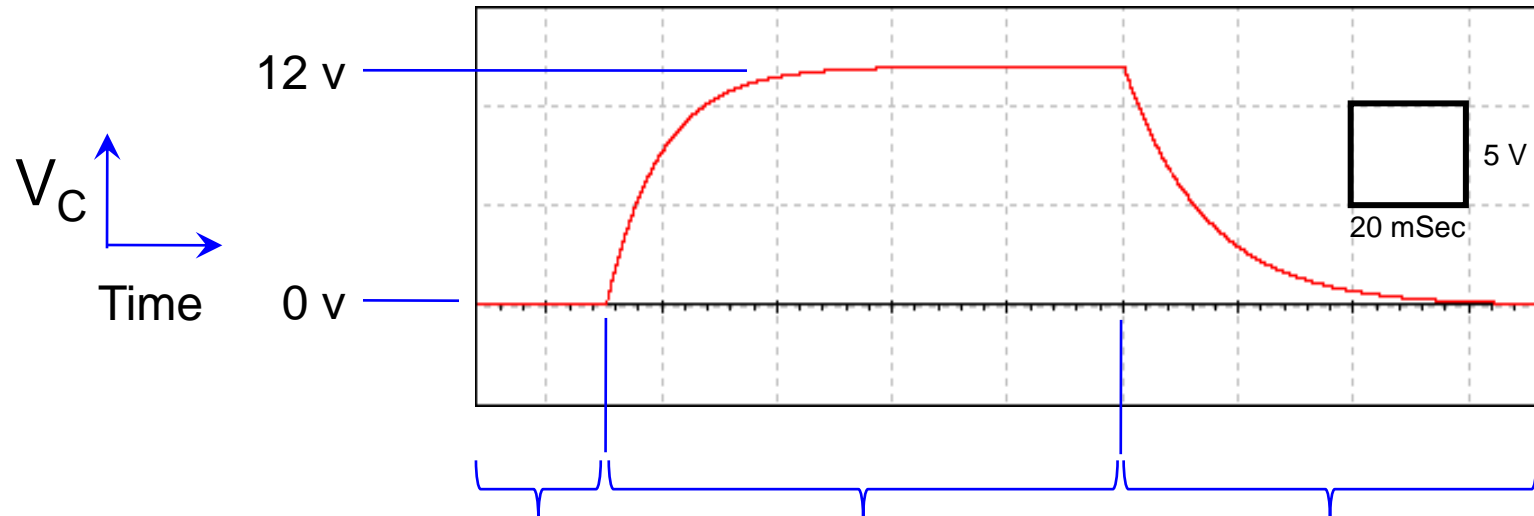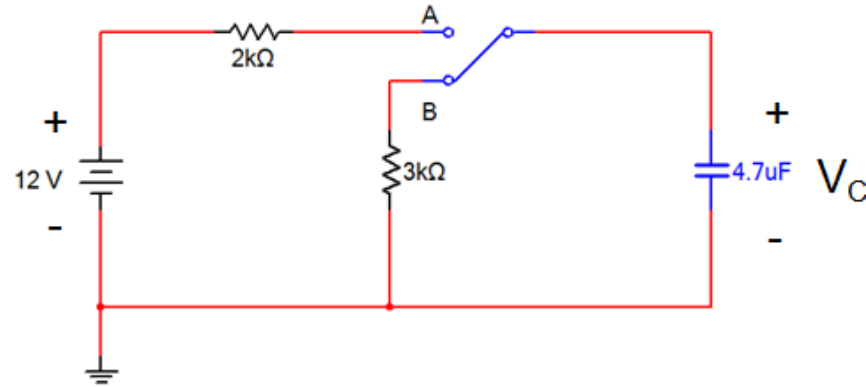


Switch has been at position B for a long period of time. The capacitor is completely discharged.


Switch is moved to position A. The capacitor charges through the 2K Ω resistor.

Switch is moved back to position B. The capacitor discharges through the 3K Ω resistors.


Reference and Comparators

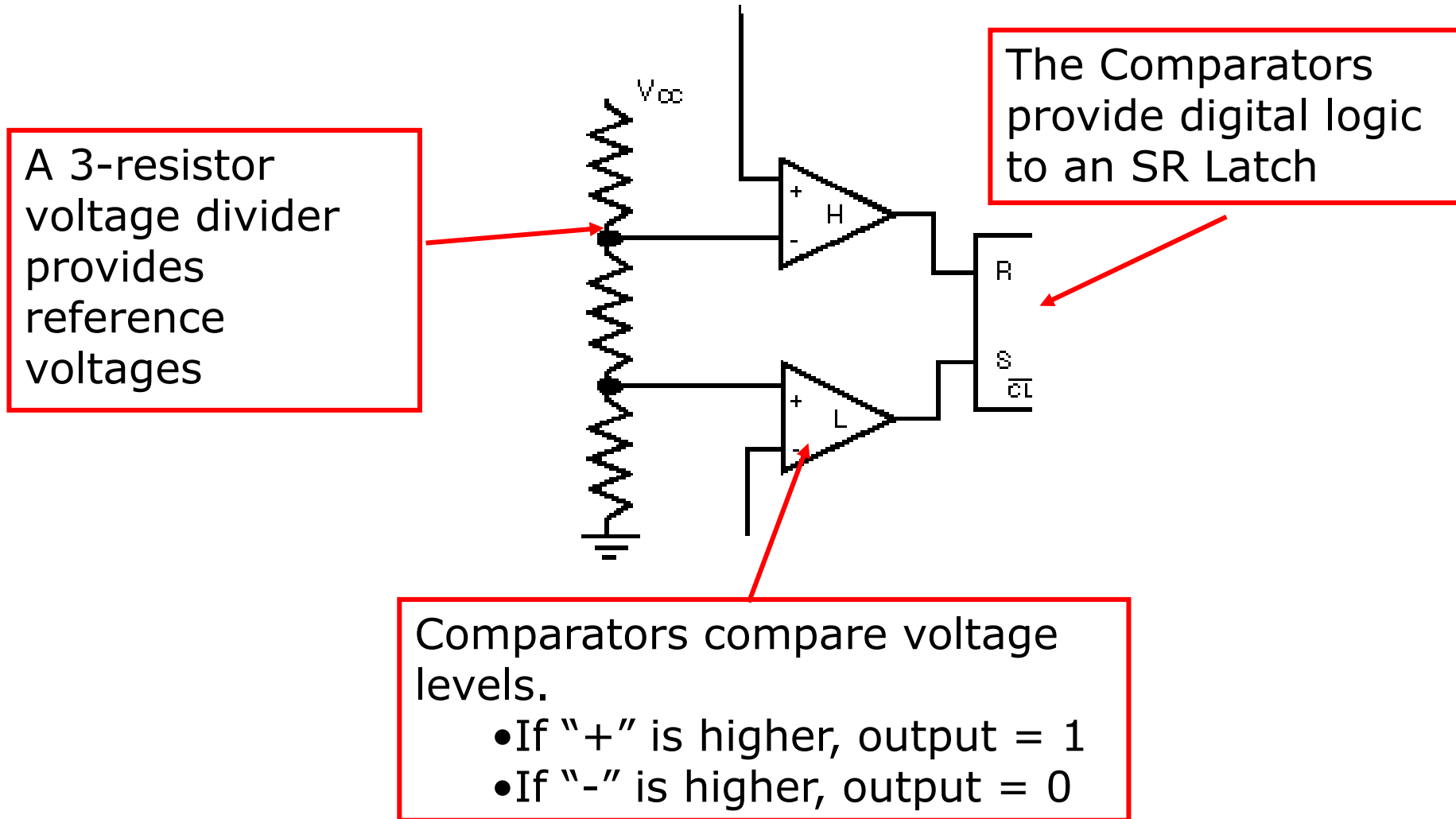

Reference and Comparators: continued..

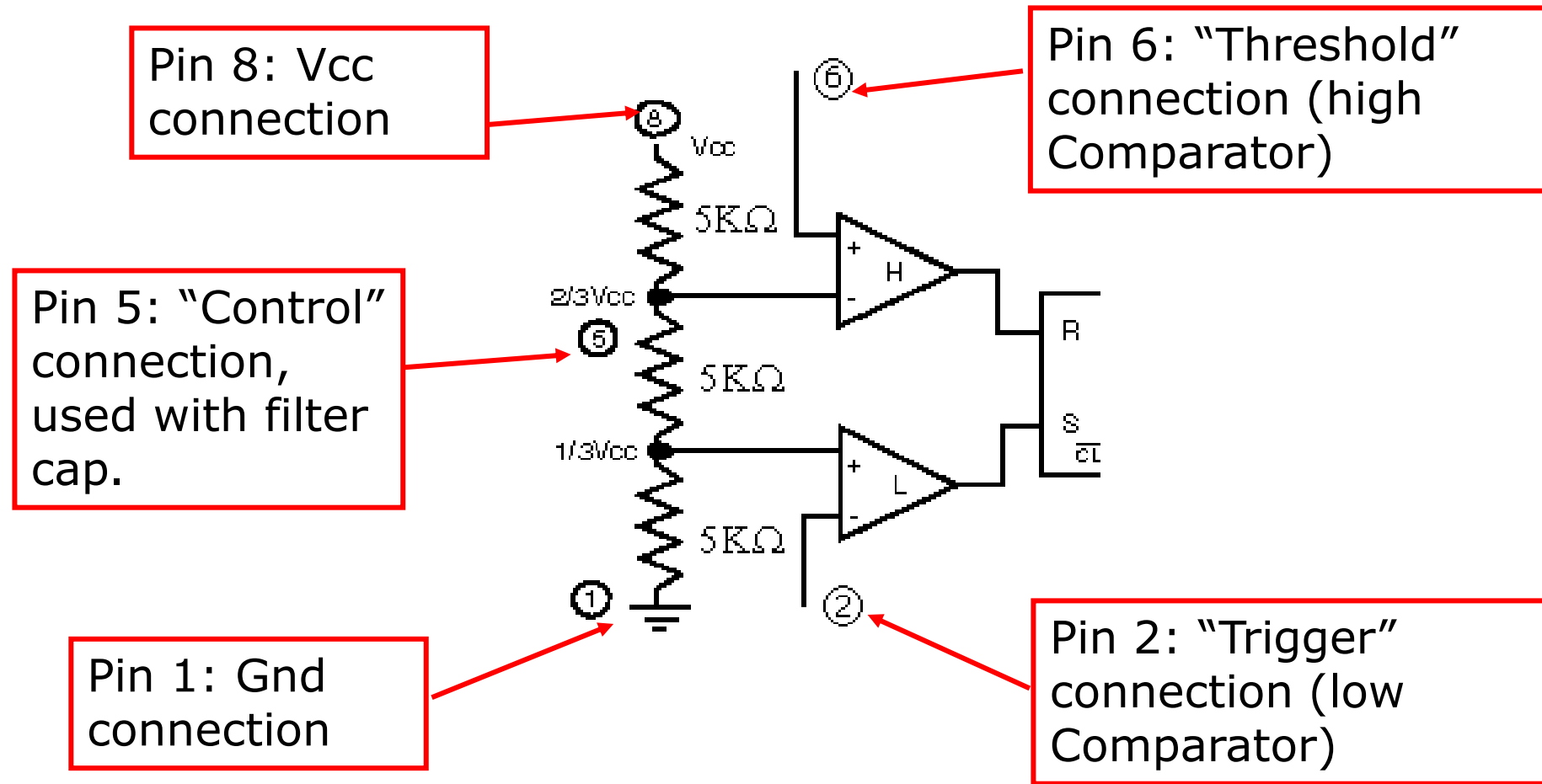

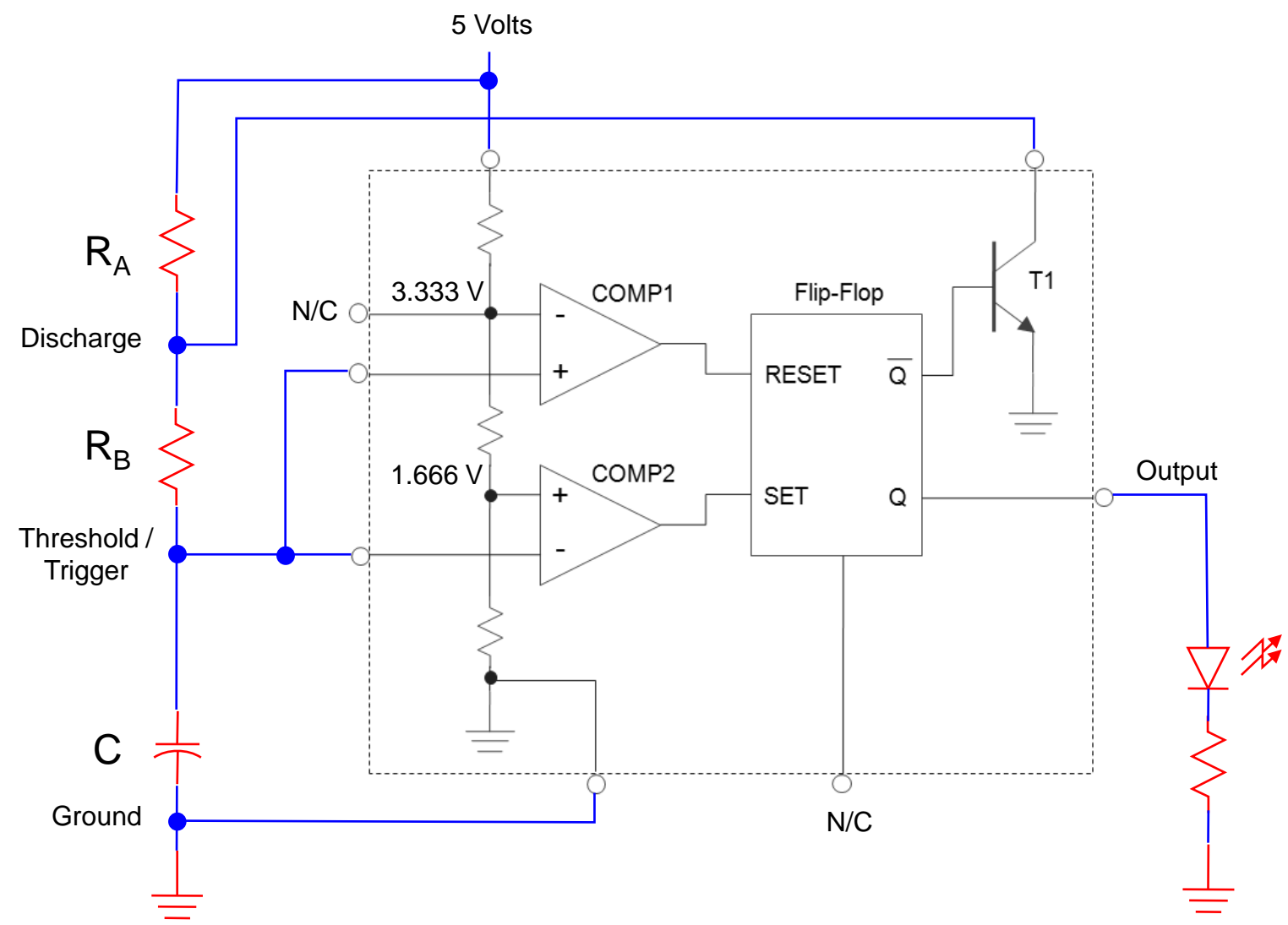
Schematic of a 555 Timer in Oscillator Mode



555 Timer Design Equations

t_{HIGH} : Calculations for the Oscillator's HIGH Time

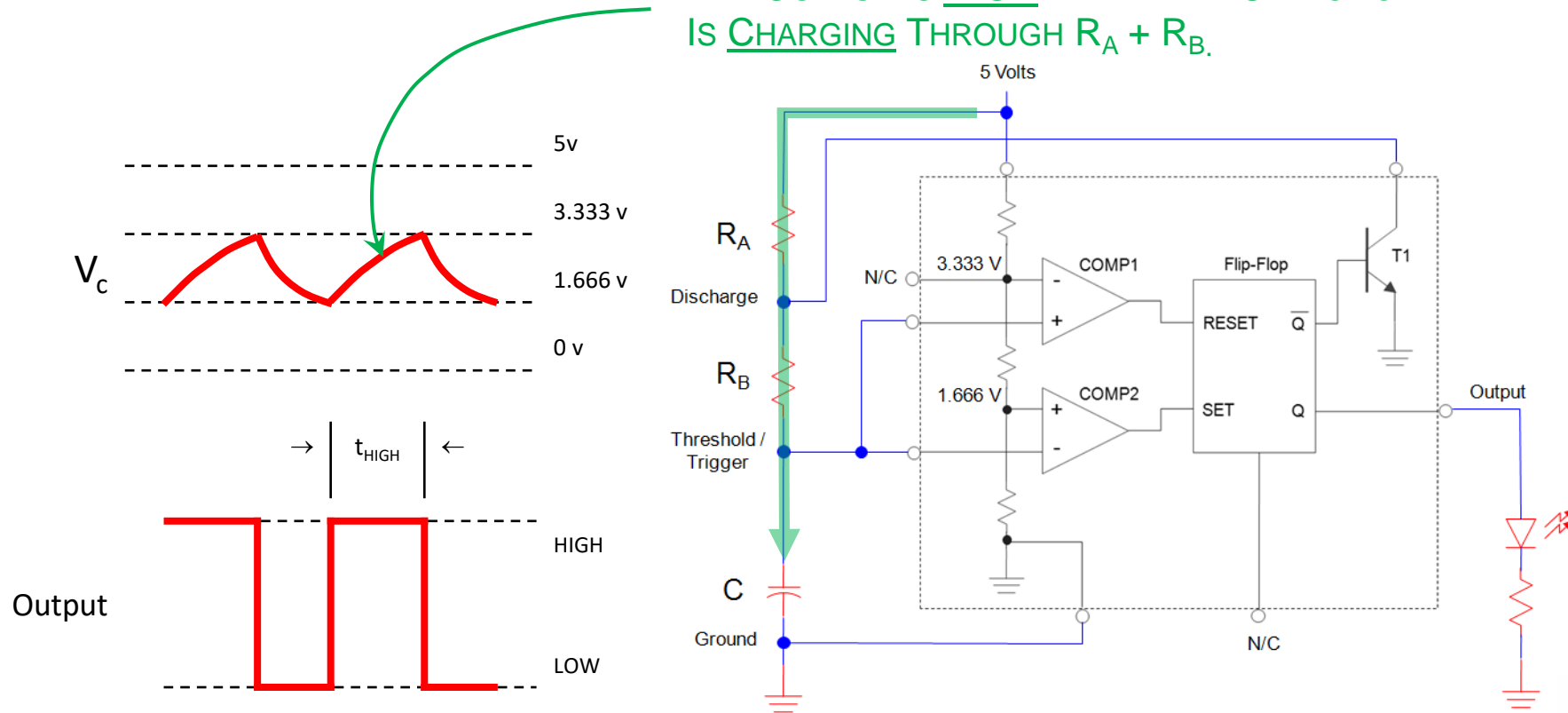
THE OUTPUT IS HIGH WHILE THE CAPACITOR IS CHARGING THROUGH $R_A + R_B$.



$$t_{\text{HIGH}} = 0.693(R_A + R_B)C$$

555 Timer Design Equations

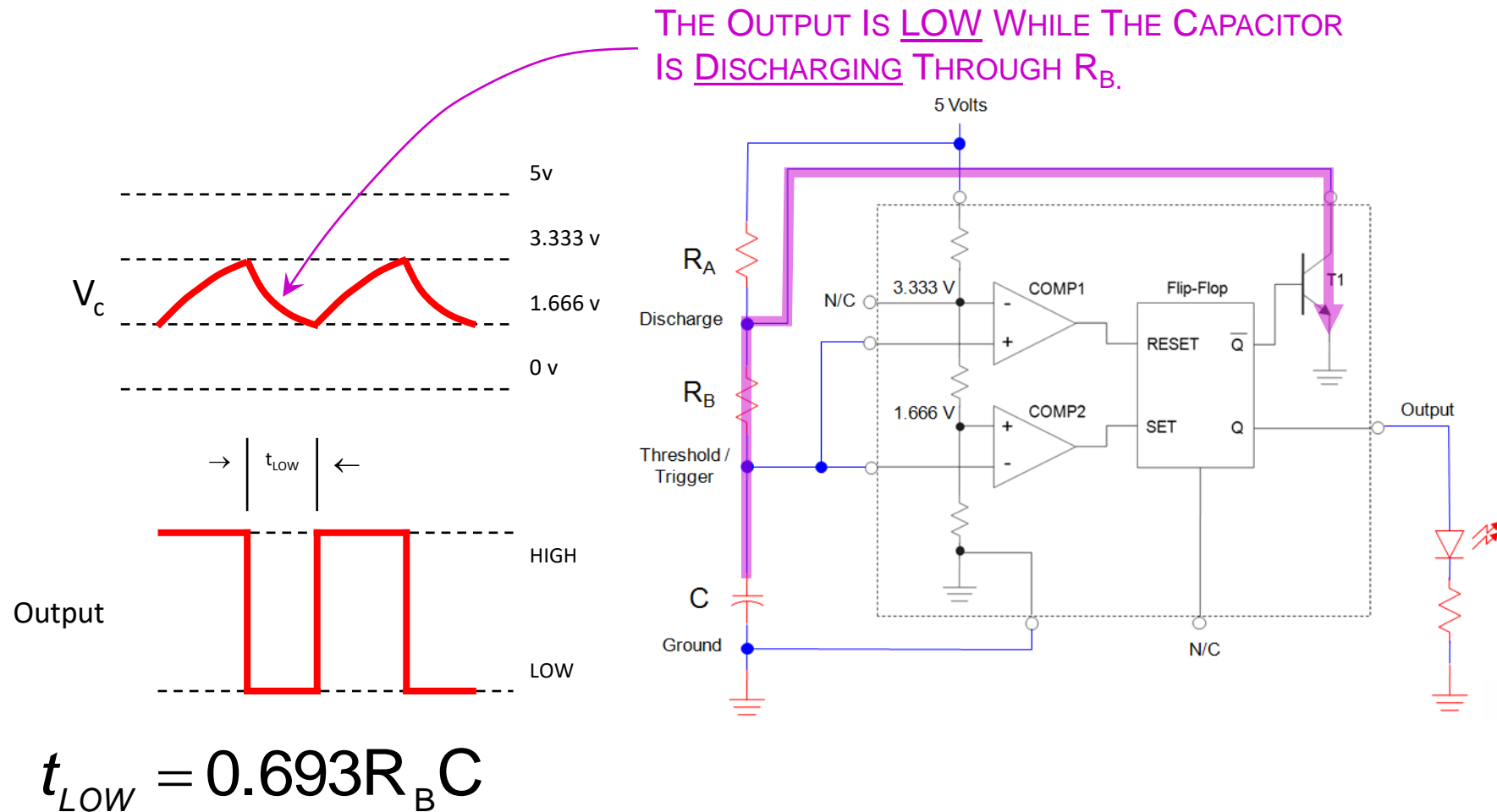t_{LOW} : Calculations for the Oscillator's LOW Time



555 Timer – Period / Frequency / DC

Period:

$$t_{\text{HIGH}} = 0.693 (R_A + R_B) C$$

$$t_{\text{LOW}} = 0.693 R_B C$$

$$T = t_{\text{HIGH}} + t_{\text{LOW}}$$

$$T = [0.693 (R_A + R_B) C] + [0.693 R_B C]$$

$$T = 0.693 (R_A + 2R_B) C$$

Duty Cycle:

$$\text{DC} = \frac{t_{\text{HIGH}}}{T} \times 100\%$$

$$\text{DC} = \frac{0.693 (R_A + R_B) C}{0.693 (R_A + 2R_B) C} \times 100\%$$

$$\text{DC} = \frac{(R_A + R_B)}{(R_A + 2R_B)} \times 100\%$$

Frequency:


$$F = \frac{1}{T}$$

$$F = \frac{1}{0.693 (R_A + 2R_B) C}$$

Example: 555 Oscillator

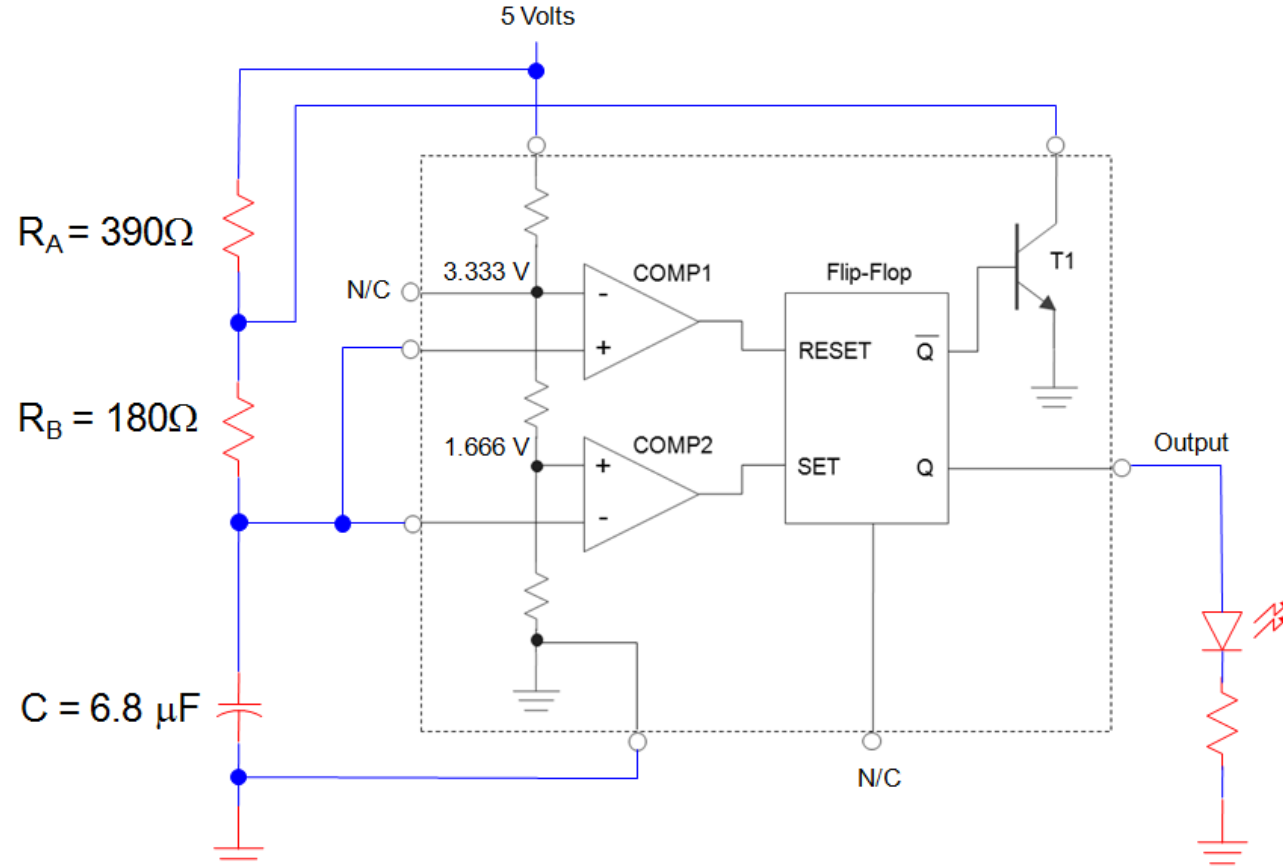Example:

For the 555 Timer oscillator shown below, calculate the circuit's, period (T), frequency (F), and duty cycle (DC).



Example: 555 Oscillator

Solution:

$$R_A = 390\ \Omega \quad R_B = 180\ \Omega \quad C = 6.8\ \mu F$$

Period:

$$T = 0.693 (R_A + 2R_B) C$$

$$T = 0.693 (390\ \Omega + 2 \times 180\ \Omega) \times 6.8\ \mu F$$

$$T = 3.534\ \text{mSec}$$

Frequency:

$$F = \frac{1}{T}$$

$$F = \frac{1}{3.534\ \text{mSec}}$$

$$F = 282.941\ \text{Hz}$$

Duty Cycle:

$$DC = \frac{(R_A + R_B)}{(R_A + 2R_B)} \times 100\%$$


$$DC = \frac{(390\ \Omega + 180\ \Omega)}{(390\ \Omega + 2 \times 180\ \Omega)} \times 100\%$$

$$DC = 76\%$$

Example: 555 Oscillator

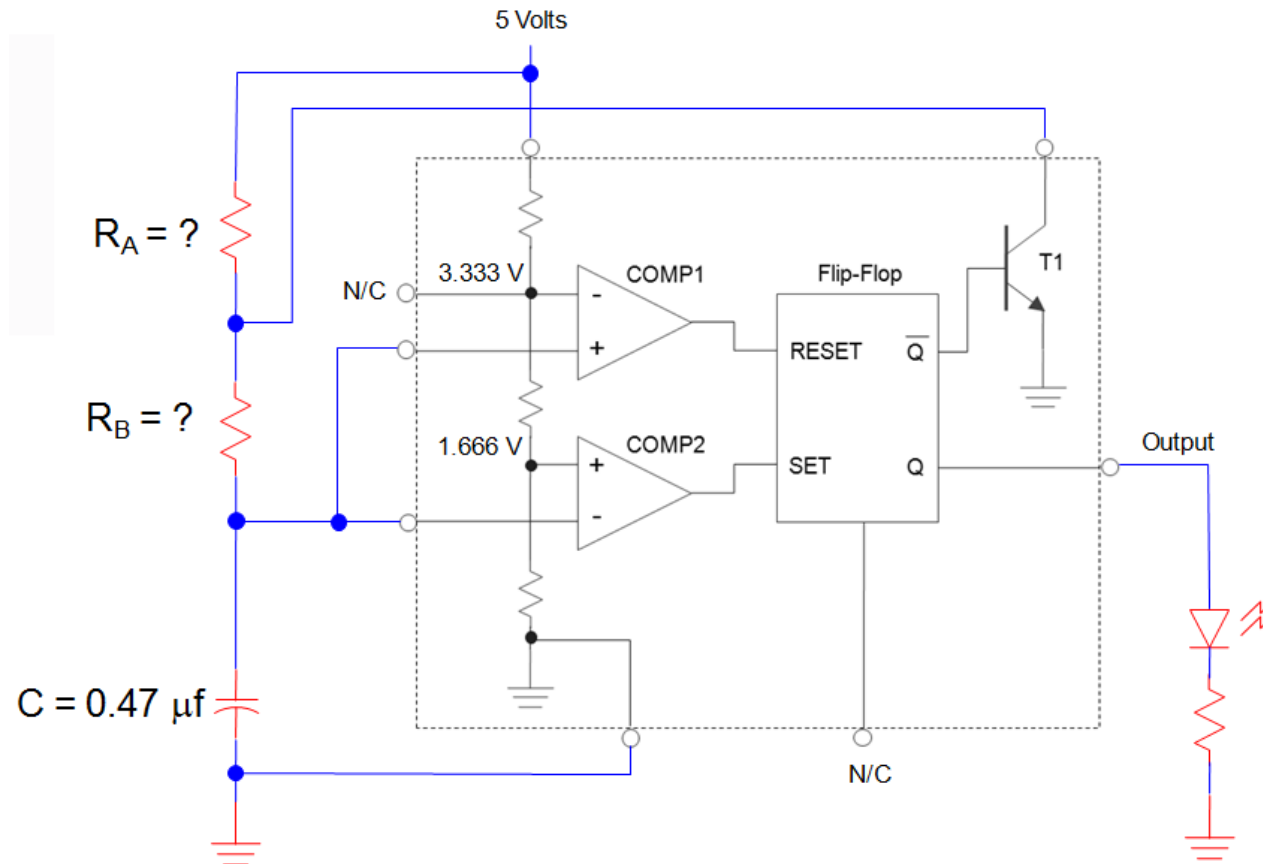Example:

For the 555 Timer oscillator shown below, calculate the value for R_A & R_B so that the oscillator has a frequency of 2.5 KHz @ 60% duty cycle.



Example: 555 Oscillator

Solution:

Frequency:

$$T = \frac{1}{f} = \frac{1}{2.5 \text{ kHz}} = 400 \mu\text{Sec}$$

$$T = 0.693 (R_A + 2R_B) C = 400 \mu\text{Sec}$$

$$T = 0.693 (R_A + 2R_B) 0.47 \mu\text{f} = 400 \mu\text{Sec}$$

$$R_A + 2R_B = \frac{400 \mu\text{Sec}}{0.693 \times 0.47 \mu\text{f}} = 1228.09 \Omega$$

$$R_A + 2R_B = 1228.09$$

Duty Cycle:

$$\text{DC} = \frac{(R_A + R_B)}{(R_A + 2R_B)} \times 100\% = 60\%$$

$$\frac{(R_A + R_B)}{(R_A + 2R_B)} = 0.6$$

$$R_A + R_B = 0.6(R_A + 2R_B)$$

$$R_A + R_B = 0.6 \times R_A + 1.2 \times R_B$$

$$0.4 \times R_A = 0.2 \times R_B$$

$$R_A = 0.5 \times R_B$$

Two Equations & Two Unknowns!

Example: 555 Oscillator

Solution:

Frequency:

$$R_A + 2R_B = 1228.09$$

Duty Cycle:

$$R_A = 0.5 \times R_B$$

Substitute and Solve for R_B

$$R_A + 2R_B = 1228.09 \Omega$$

$$0.5 \times R_B + 2R_B = 1228.09 \Omega$$

$$2.5R_B = 1228.09 \Omega$$

$$R_B = 491.23 \Omega$$

Substitute and Solve for R_A



$$R_A + 2R_B = 1228.09 \Omega$$

$$R_A + 2(491.23 \Omega) = 1228.09 \Omega$$



$$R_A + 982.472 \Omega = 1228.09 \Omega$$

$$R_A = 245.618 \Omega$$

Detail Analysis of a 555 Oscillator

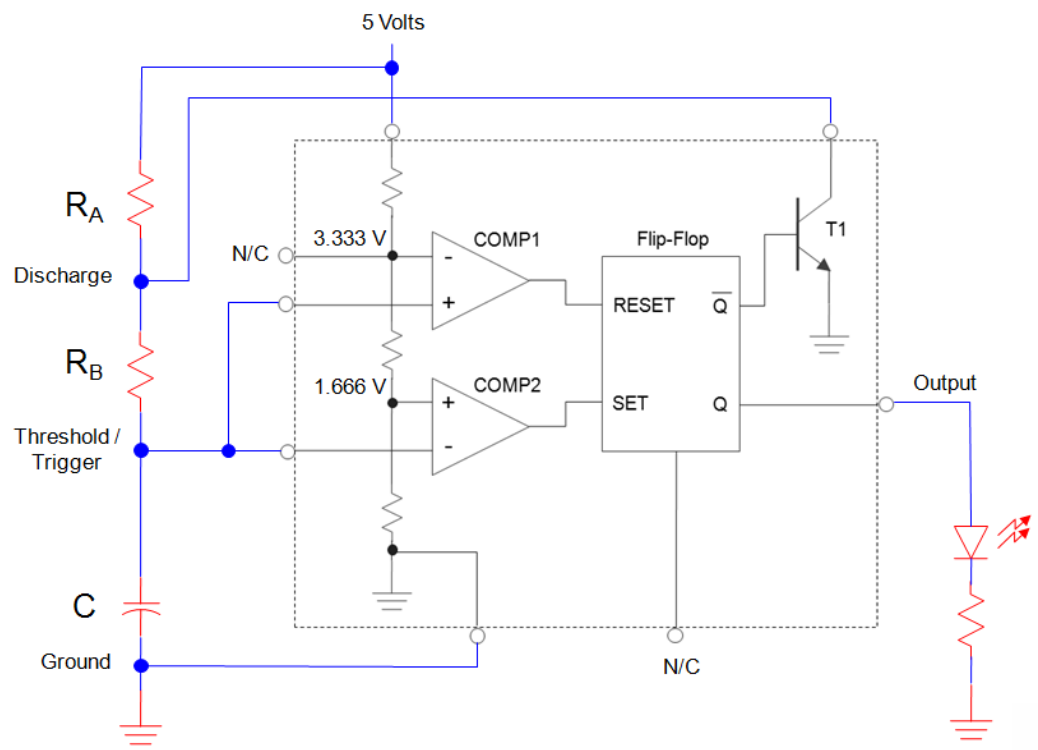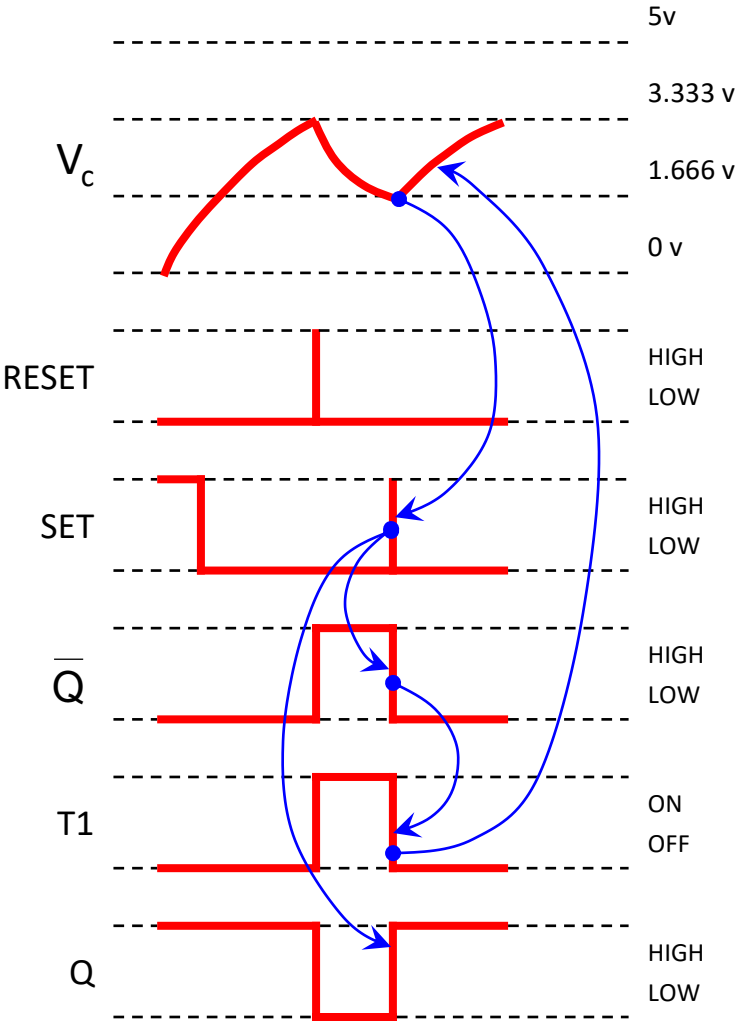

Detail Analysis of a 555 Oscillator

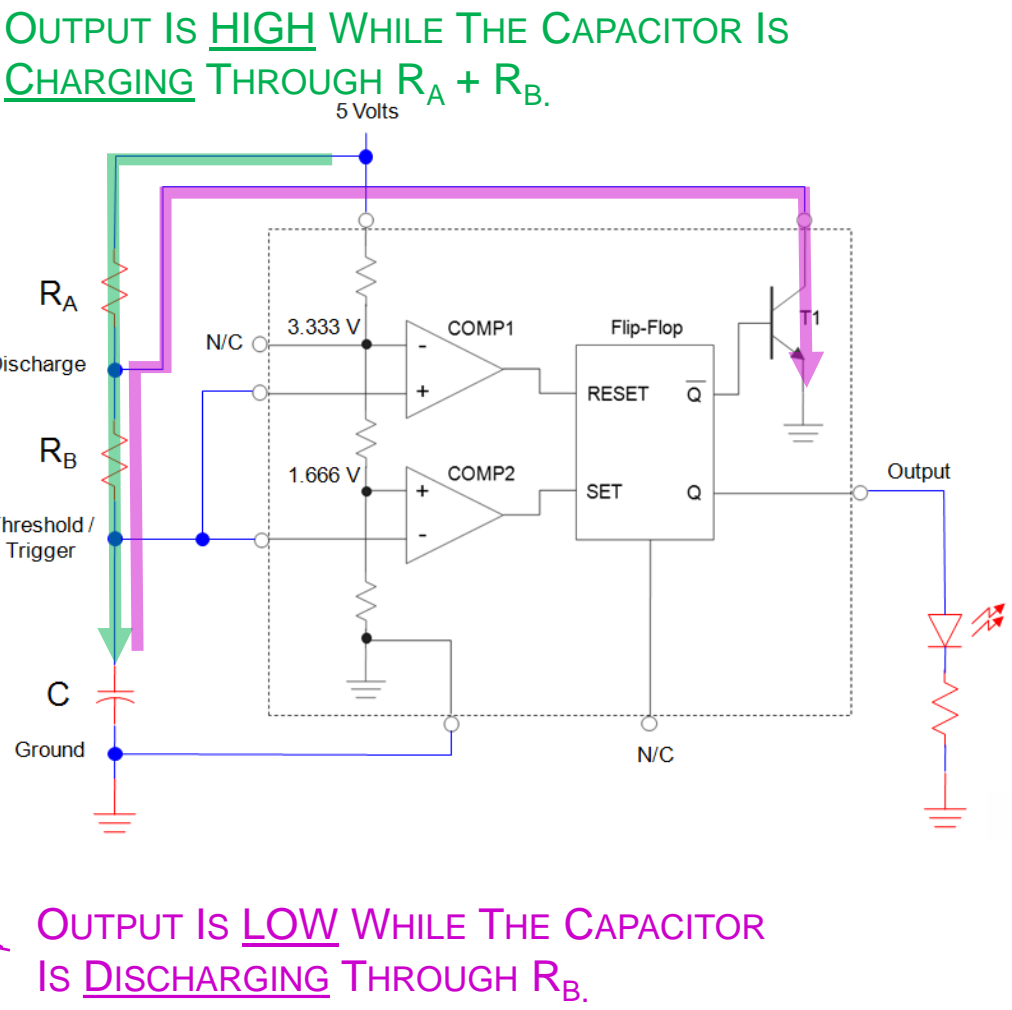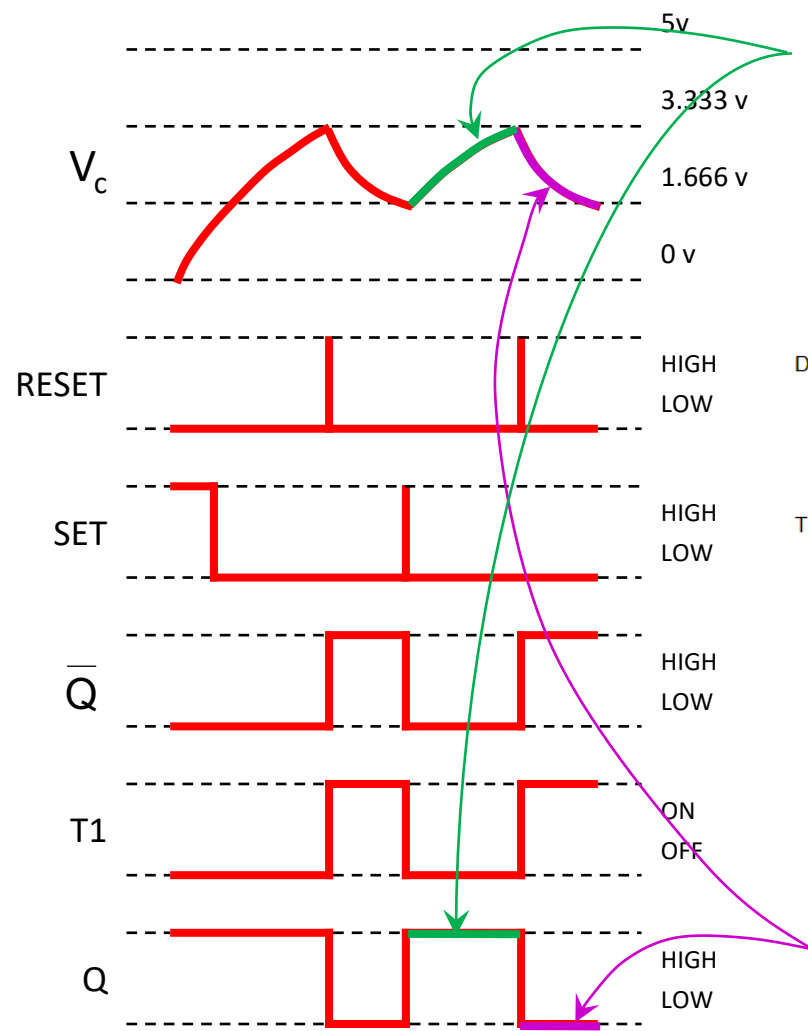

555 Timer Design Equations

t_{HIGH} : Calculations for the Oscillator's HIGH Time

$$V_C = (V_{\text{Final}} - V_{\text{Initial}}) \times \left(1 - e^{-\frac{t}{RC}}\right) + V_{\text{Initial}} \quad \rightarrow \quad \frac{1}{2} = \left(1 - e^{-\frac{t}{RC}}\right)$$

$$\frac{2}{3} V_{CC} = \left(V_{CC} - \frac{1}{3} V_{CC}\right) \times \left(1 - e^{-\frac{t}{RC}}\right) + \frac{1}{3} V_{CC} \quad - \frac{1}{2} = -e^{-\frac{t}{RC}}$$

$$\frac{2}{3} V_{CC} = \left(\frac{2}{3} V_{CC}\right) \times \left(1 - e^{-\frac{t}{RC}}\right) + \frac{1}{3} V_{CC} \quad \ln\left(\frac{1}{2}\right) = \ln\left(e^{-\frac{t}{RC}}\right)$$

$$\frac{\frac{2}{3} V_{CC} - \frac{1}{3} V_{CC}}{\frac{2}{3} V_{CC}} = \left(1 - e^{-\frac{t}{RC}}\right) \quad -0.693 = -\frac{t}{RC}$$

$$\frac{1}{2} = \left(1 - e^{-\frac{t}{RC}}\right) \quad t_{\text{HIGH}} = 0.693 R C$$

$$t_{\text{HIGH}} = 0.693(R_A + R_B)C$$

555 Timer Design Equations

t_{LOW} : Calculations for the Oscillator's LOW Time

$$V_C = (V_{\text{Initial}} - V_{\text{Final}}) \times \left(e^{-\frac{t}{RC}} \right)$$

$$\frac{1}{3} V_{\text{CC}} = \left(\frac{2}{3} V_{\text{CC}} - 0 \right) \times \left(e^{-\frac{t}{RC}} \right)$$

$$\frac{1}{3} V_{\text{CC}} = \left(\frac{2}{3} V_{\text{CC}} \right) \times \left(e^{-\frac{t}{RC}} \right)$$

$$\frac{\frac{1}{3} V_{\text{CC}}}{\frac{2}{3} V_{\text{CC}}} = \left(e^{-\frac{t}{RC}} \right)$$

$$\frac{1}{2} = \left(e^{-\frac{t}{RC}} \right)$$

$$\frac{1}{2} = \left(e^{-\frac{t}{RC}} \right)$$

$$\ln\left(\frac{1}{2}\right) = \ln\left(e^{-\frac{t}{RC}} \right)$$

$$-0.693 = -\frac{t}{RC}$$

$$t_{\text{LOW}} = 0.693 R$$

$$t_{\text{LOW}} = 0.693 R_B C$$

555 Timer – Period / Frequency / DC

Period:

$$t_{\text{HIGH}} = 0.693 (R_A + R_B) C$$

$$t_{\text{LOW}} = 0.693 R_B C$$

$$T = t_{\text{HIGH}} + t_{\text{LOW}}$$

$$T = [0.693 (R_A + R_B) C] + [0.693 R_B C]$$

$$T = 0.693 (R_A + 2R_B) C$$

Duty Cycle:

$$\text{DC} = \frac{t_{\text{HIGH}}}{T} \times 100\%$$

$$\text{DC} = \frac{0.693 (R_A + R_B) C}{0.693 (R_A + 2R_B) C} \times 100\%$$


$$\text{DC} = \frac{(R_A + R_B)}{(R_A + 2R_B)} \times 100\%$$

Frequency:

$$F = \frac{1}{T}$$


$$F = \frac{1}{0.693 (R_A + 2R_B) C}$$

555 Layout

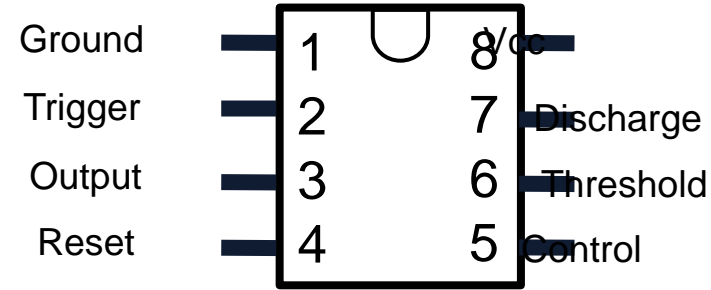

Also available:

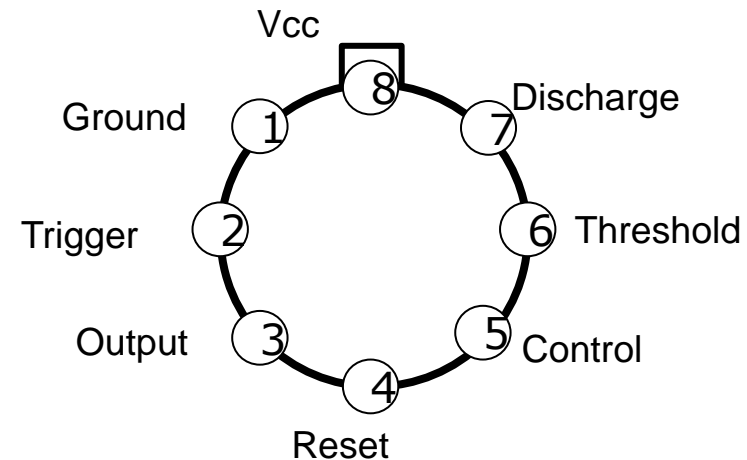- 556 (two-555's in one DIP package)
- 555 in a "metal can" configuration



Astable Multivibrator using 555

The positive output is high for T_H seconds based on this formula:

$$T_H(\text{sec}) = 0.693 \times (R1 + R2) \times C$$

The negative output is low for T_L seconds based on this formula:

$$T_L(\text{sec}) = 0.693 \times R2 \times C$$

The frequency is derived by the formula:

$$f = \frac{1.44}{(R1 + R2 + R3) \times C}$$

The duty cycle percentage is the relationship of the high time to the overall cycle time.

